

Literature:

MOSFET: p 292-318

Transistor amplifier: P 350-431

Frequency response: p 649 – 675

Assignments:

8.1:

A MOSFET circuit is shown in Fig. 1. It is assumed that: $V_{DD} = 10\text{ V}$, $R_G = 33\text{ K}\Omega$, $R_D = 5.6\text{ K}\Omega$ and the channel length modulation coefficient $\lambda = 0$. Furthermore, we assume that $V_{TH} = 2\text{ V}$ and $k_n = 0.9 \cdot 10^{-3}\text{ A/V}^2$.

- (a) To achieve $I_D = 1\text{ mA}$, $V_{GS} = ?$
- (b) To have V_{GS} obtained in (a), $V_{BB} = ?$ Explain why.
- (c) To ensure the MOSFET operating in saturation, how large is the output signal swing?
- (d) Setup a small signal circuit and calculate the component values and voltage gain A_v .
- (e) To achieve a maximum output signal swing for $I_D = 1\text{ mA}$, $R_D = ?$
- (f) If the channel length modulation coefficient $\lambda = 0.5$ and $R_D = 5.6\text{ K}\Omega$ are considered, the output resistance $r_o = ?$ The voltage gain $A_v = ?$

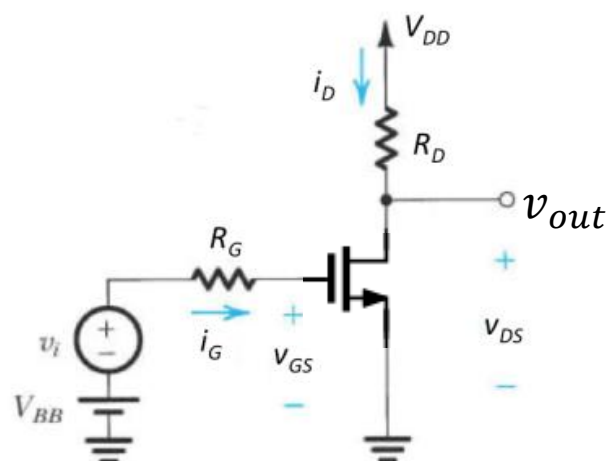


Fig. 1 A MOSFET circuit

8.2:

A common gate amplifier is given in Fig.2.

- (a) Draw the internal capacitors of the circuit.
- (b) Simplify the circuit by merging the capacitors.
- (c) Is there any floating capacitor in the circuit?
- (d) If yes, how to decompose the floating capacitor into two capacitors connected to AC ground by using Millers theorem?

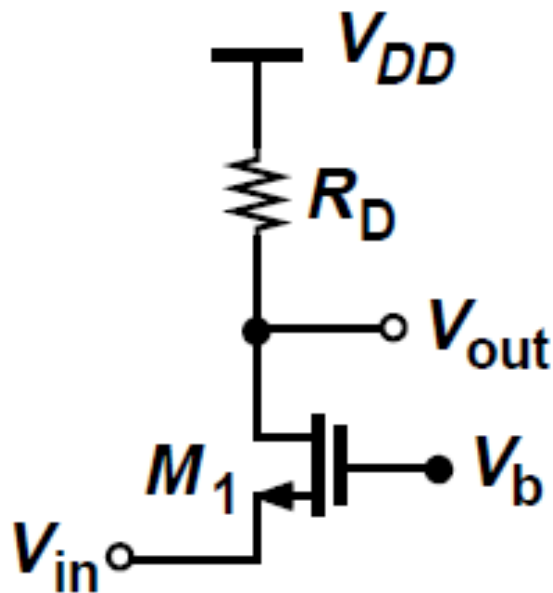


Fig. 2 A common gate amplifier