

Lec. 1: assignment 1.1

In the laboratory, 2 sets of related values of current and voltage at two temperatures have been measured for the diode 1N4001:

- At 25°C : $(V_{D1}, I_{D1}) = (540 \text{ mV}, 1\text{mA})$, and $(V_{D2}, I_{D2}) = (450 \text{ mV}, 0.1\text{mA})$
 - At 75°C: $(V_{D1}, I_{D1}) = (420 \text{ mV}, 1\text{mA})$, and $(V_{D2}, I_{D2}) = (315 \text{ mV}, 0.1\text{mA})$
- Calculate the constants of the diode equation: n and I_s for each temperature.
 - Calculate the temperature coefficient [mV/K] of the diode at current = 1 mA.

$$I_D \approx I_s e^{\frac{V_D}{nV_T}}$$

$$V_D = nV_T \ln \frac{I_D}{I_s}$$


$$V_{D2} = nV_T \ln \frac{I_{D2}}{I_s} \text{ \& } V_{D1} = nV_T \ln \frac{I_{D1}}{I_s} \rightarrow n = \frac{V_{D2} - V_{D1}}{V_T \ln \frac{I_{D2}}{I_{D1}}} \text{ \& } I_s = I_{D1} e^{-\frac{V_{D1}}{nV_T}}$$

$$V_T = \frac{KT_K}{q} \rightarrow V_T(25^\circ\text{C}) = 25.7 \text{ mV} \text{ \& } V_T(75^\circ\text{C}) = 30 \text{ mV}$$


$$\text{At } 25^\circ\text{C: } n = \frac{450 \text{ mV} - 540 \text{ mV}}{25.7 \text{ mV} \ln \frac{0.1 \text{ mA}}{1 \text{ mA}}} = 1.52 \text{ \& } I_s = 1 \text{ mA} e^{-\frac{540 \text{ mV}}{1.52 * 25.7 \text{ mV}}} = 1 \text{ nA}$$

$$\text{At } 75^\circ\text{C: } n = \frac{315 \text{ mV} - 420 \text{ mV}}{30.0 \text{ mV} \ln \frac{0.1 \text{ mA}}{1 \text{ mA}}} = 1.52 \text{ \& } I_s = 1 \text{ mA} e^{-\frac{420 \text{ mV}}{1.52 * 30.0 \text{ mV}}} = 100 \text{ nA}$$

$$\frac{\Delta V_D}{\Delta T} = \frac{420 \text{ mV} - 540 \text{ mV}}{75^\circ\text{C} - 25^\circ\text{C}} = -2.4 \text{ mV}/^\circ\text{C}$$

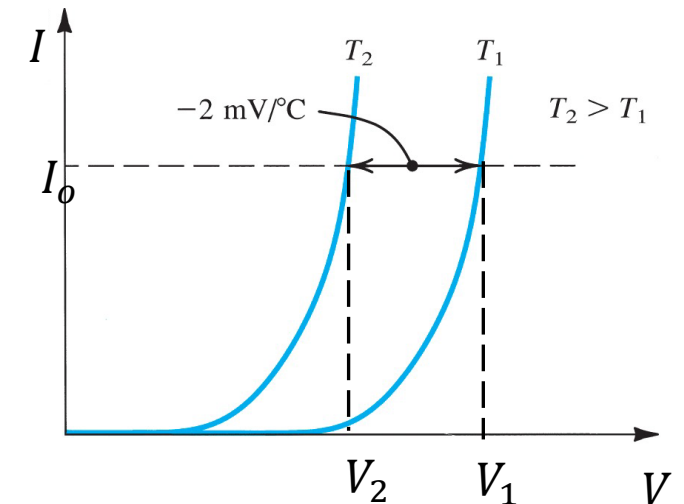


Lec. 1: assignment 1.2

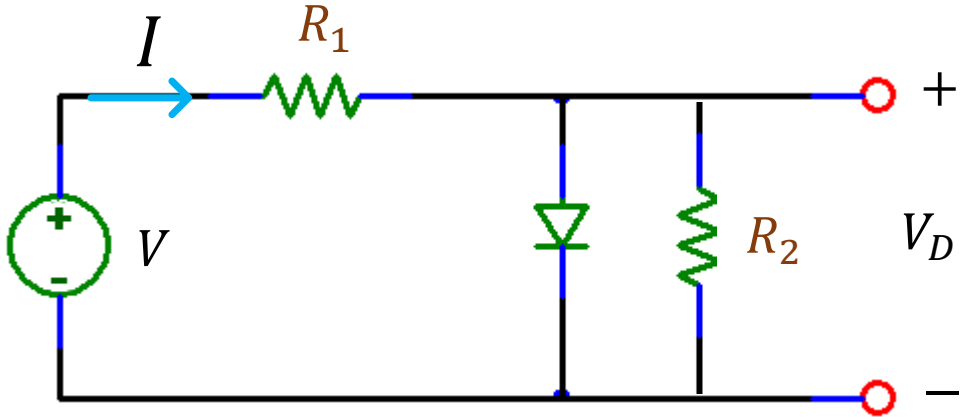

1. The ideal model
 - a. Draw the equivalent circuit and calculate I , I_{R_2} , V_{R_1} , V_D and V_{R_2}
 - When $V < 0$
 - When $V = 0$
 - When $V > 0$
 - b. The I-V curve.
 - c. The I_{R_2} -V curve.
 - d. The I_D -V curve.
 - e. The V_{R_1} -V curve, with V_{R_1} denoting the voltage across R_1 .
 - f. The V_D -V curve, with V_D denoting the voltage across diode.


Lec. 1: assignment 1.2 –ideal model

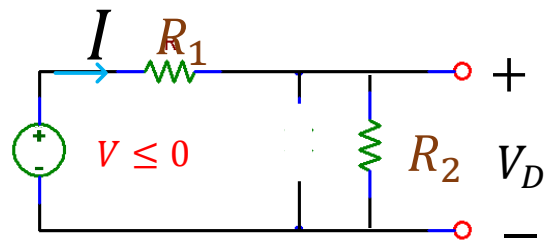

$$I = I_{R_2} = V / (R_1 + R_2)$$

$$V_{R1} = V R_1 / (R_1 + R_2)$$

$$V_D = V_{R2} = V R_2 / (R_1 + R_2)$$




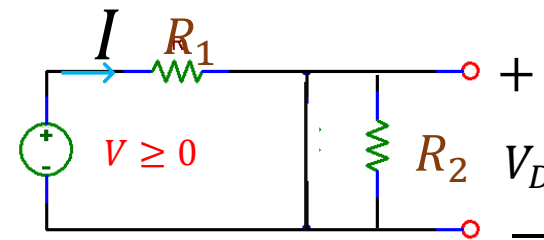


$$I = V / R_1$$


$$I_{R_2} = 0$$

$$V_{R1} = I R_1 = V$$

$$V_D = V_{R2} = 0$$

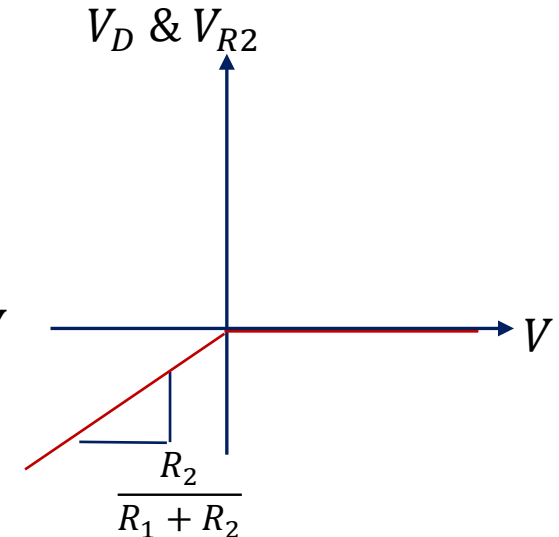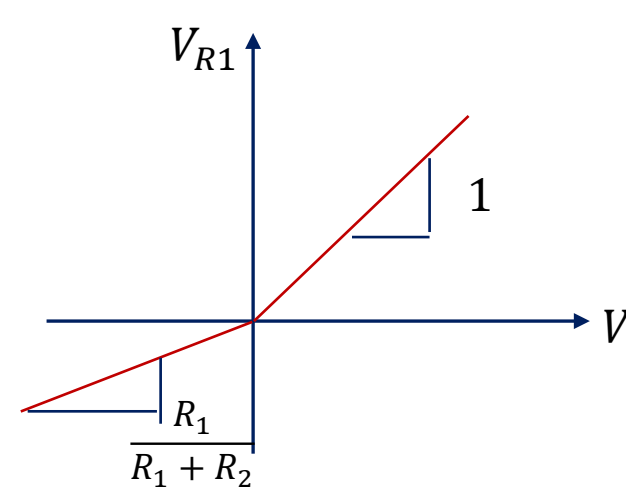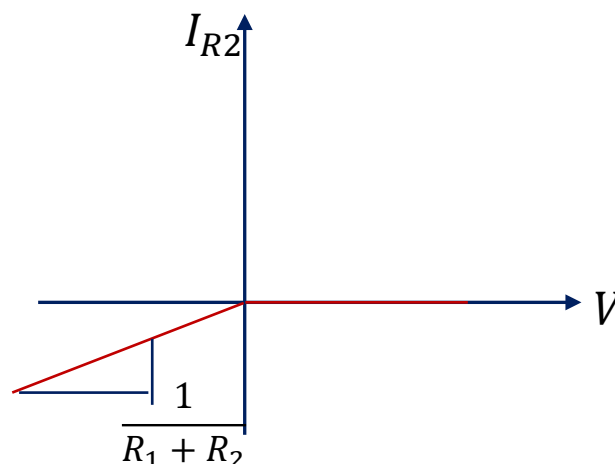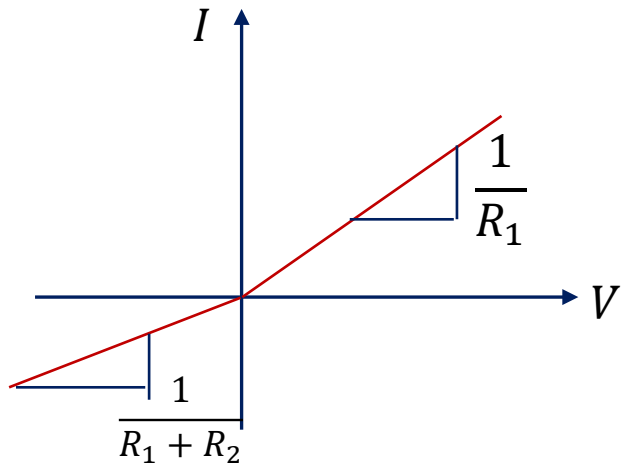

Lec. 1: assignment 1.2

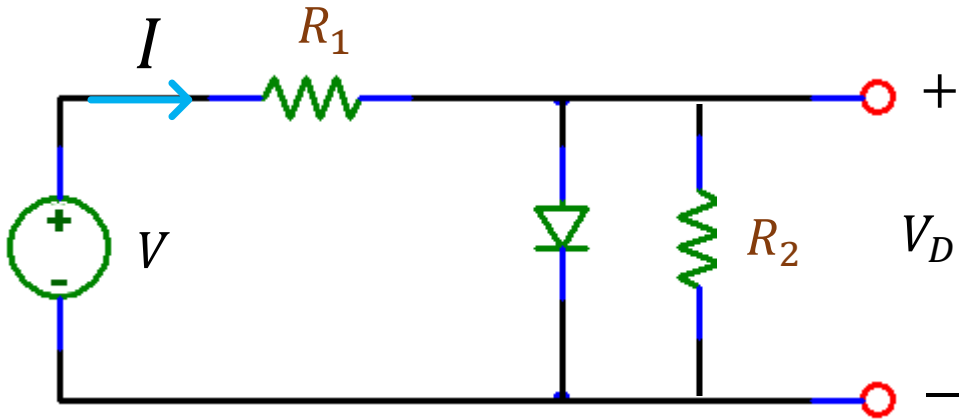


2. Constant voltage drop model

Draw the equivalent circuit and calculate I , I_{R_2} , V_{R1} , V_D and V_{R2}

- When $V < V_{D,on}$
 - When $V = V_{D,on}$
 - When $V = \frac{R_1 + R_2}{R_2} V_{D,on}$
 - When $V > \frac{R_1 + R_2}{R_2} V_{D,on}$
- a. The I-V curve.
 - b. The I_{R_2} -V curve.
 - c. The I_D -V curve.
 - d. The V_{R1} -V curve, with V_{R1} denoting the voltage across R_1 .
 - e. The V_D -V curve, with V_D denoting the voltage across diode.

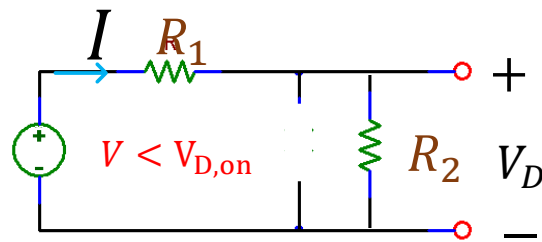Lec. 1: assignment 1.2 –constant voltage drop




$$V < V_{D,on}$$

$$I = I_{R_2} = V / (R_1 + R_2)$$

$$V_{R1} = V R_1 / (R_1 + R_2)$$

$$V_D = V_{R2} = V R_2 / (R_1 + R_2)$$

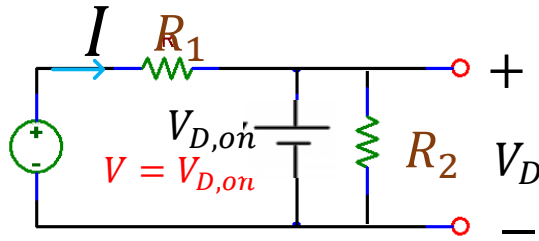

If we assume $V = V_{D,on}$, the diode is on \rightarrow the voltage drop across R_1 will be 0 $\rightarrow I = 0$ (1)

The diode is about to turn on $\rightarrow I_D = 0$

However, $I_{R2} = \frac{V_{D,on}}{R_2} \neq 0$

And $I = I_D + I_{R2} \neq 0$ (2)


(1) And (2) conflicts \rightarrow the diode should be off \rightarrow same results as for $V < V_{D,on}$

$$I = I_{R_2} = V / (R_1 + R_2)$$

$$V_{R1} = V R_1 / (R_1 + R_2)$$

$$V_D = V_{R2} = V R_2 / (R_1 + R_2)$$

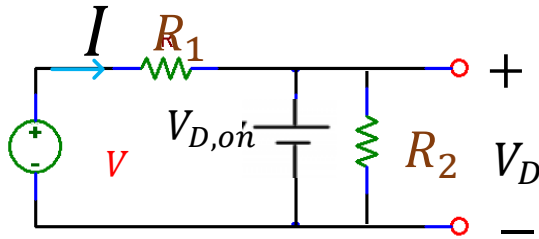Lec. 1: assignment 1.2 –constant voltage drop



$$V = \frac{R_1 + R_2}{R_2} V_{D,on}$$

If we assume $V = V_{D,on}$, the diode is on $\rightarrow I = \frac{V - V_{D,on}}{R_1} = \frac{V_{D,on}}{R_2}$

(1)

The diode is about to turn on $\rightarrow I_D = 0$

$$\text{And, } I_{R2} = \frac{V_{D,on}}{R_2}$$

$$\text{And } I = I_D + I_{R2} = \frac{V_{D,on}}{R_2} \quad (2)$$


(1) And (2) true \rightarrow the diode should be on

$$I = I_{R2} = \frac{V_{D,on}}{R_2}$$

$$V_{R1} = IR_1 = \frac{R_1 V_{D,on}}{R_2}$$

$$V_D = V_{R2} = V_{D,on}$$

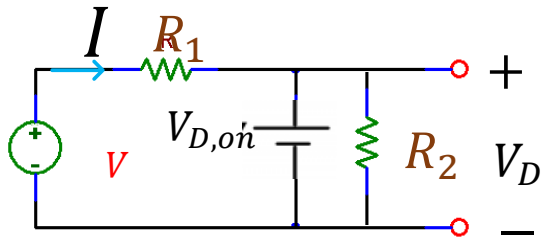Lec. 1: assignment 1.2 –constant voltage drop



$$V > \frac{R_1 + R_2}{R_2} V_{D,on}$$

$$\text{the diode is on} \rightarrow I = \frac{V - V_{D,on}}{R_1}$$






$$I_{R2} = \frac{V_{D,on}}{R_2}$$

$$I_D = I - I_{R2} = \frac{V - V_{D,on}}{R_1} - \frac{V_{D,on}}{R_2}$$


$$V_{R1} = IR_1 = V - V_{D,on}$$

$$V_D = V_{R2} = V_{D,on}$$

Lec. 1: assignment 1.2 –constant voltage drop

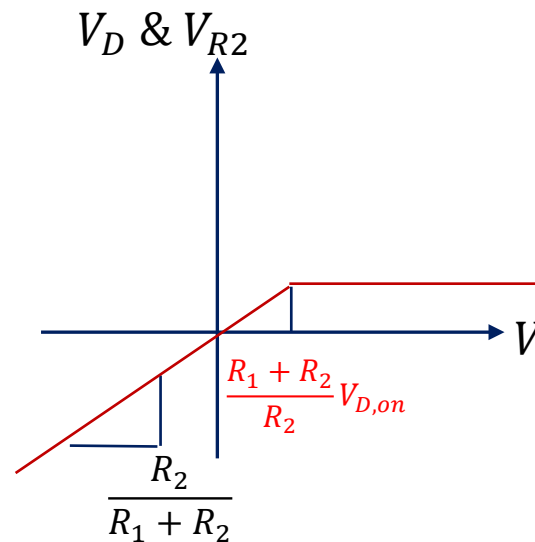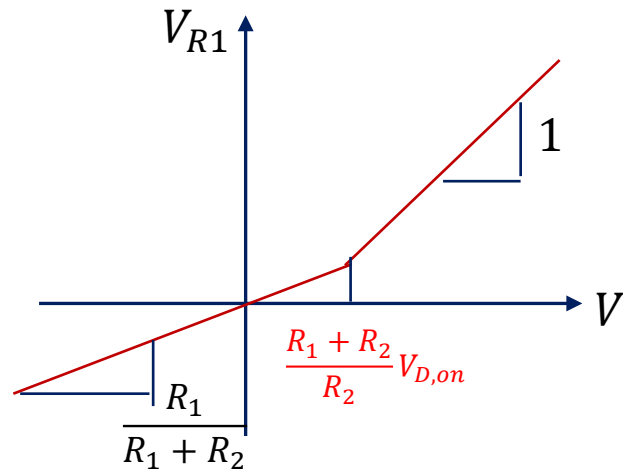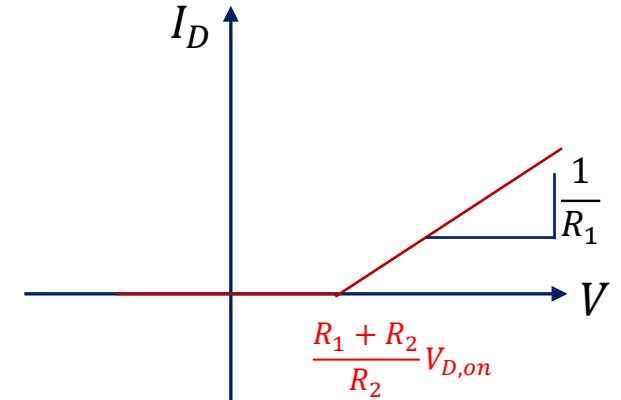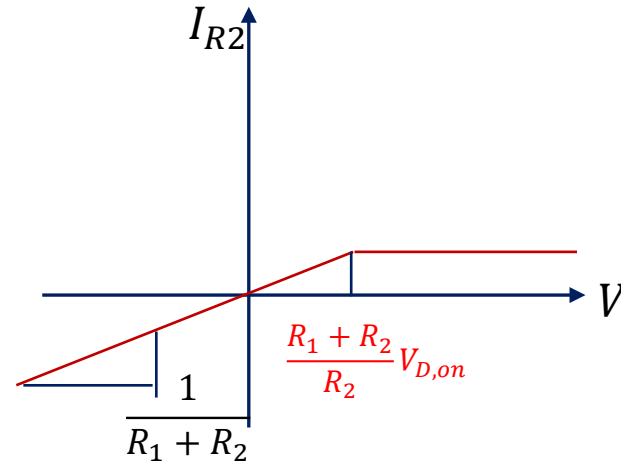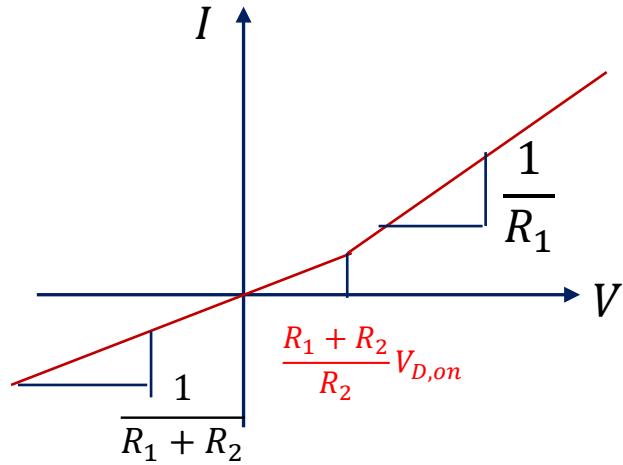

Lec. 1: assignment 1.3

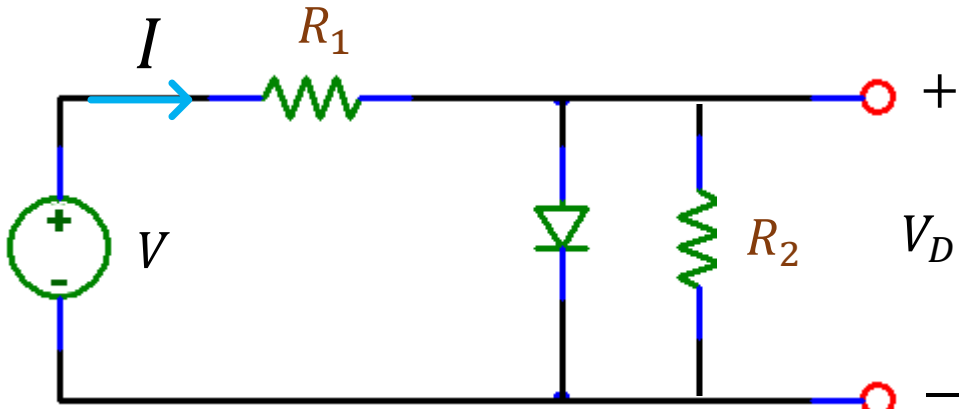

Assuming the constant voltage drop model and the diode in reverse and forward bias regions,

- The I - V curve.
- The I_{R2} - V curve.
- The I_D - V curve.
- The V_{R1} - V curve, with V_{R1} denoting the voltage across R_1 .
- The V_D - V curve, with V_D denoting the voltage across diode.
- The V_{R2} - V curve, with V_{R2} denoting the voltage across R_2 .

