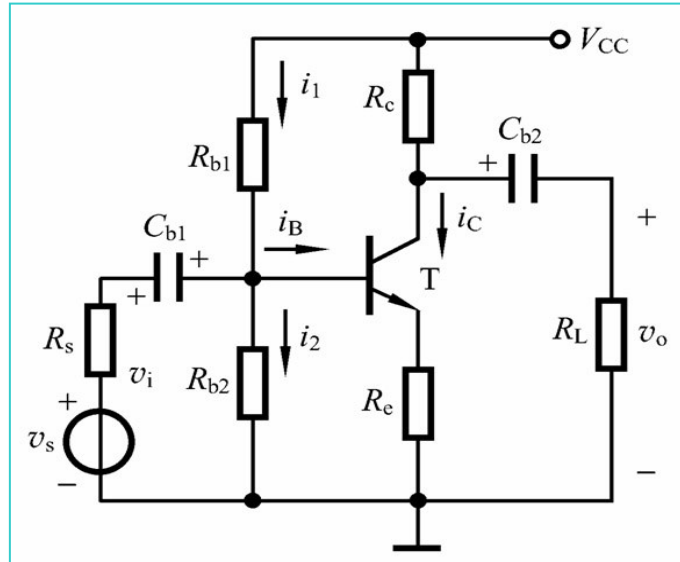


Practice Exercise _Lecture 4

1. For the following circuit, $V_{CC} = 16\text{ V}$, $R_{b1} = 56\text{ k}\Omega$, $R_{b2} = 20\text{ k}\Omega$, $R_e = 2\text{ k}\Omega$, $R_c = 3.3\text{ k}\Omega$, $R_L = 6.2\text{ k}\Omega$, $R_s = 500\text{ }\Omega$, $\beta = 80$, $V_{BEQ} = 0.7\text{ V}$.



- Draw its corresponding DC circuit, and calculate the Q operating point.
- Draw its corresponding small-signal model, and calculate R_i , R_o , and A_v .
- If a capacitor with a value of $50\mu\text{F}$ is parallel with R_e , please calculate (a) and (b) again.