

Literature:

Feedback: P 755-836

Assignments:

10.1:

A CE stage circuit without (by setting $R_f = 0$) or with feedback (by setting $R_f = 20 \Omega$) is shown in Fig. 1.

- (1) Set $R_f = 0$, i.e., without negative feedback, run the simulation and find out $A_v = ?$
 $f_L = ?$ $f_H = ?$ THD = ? @ 20KHz.
- (2) Set $R_f = 20$, i.e., with negative feedback, run the simulation and find out $A_v = ?$
 $f_L = ?$ $f_H = ?$ THD = ? @ 20KHz.
- (3) Comparing the results obtained in (1) and (2), discuss what is the advantages and disadvantages by introducing negative feedback into the circuit.

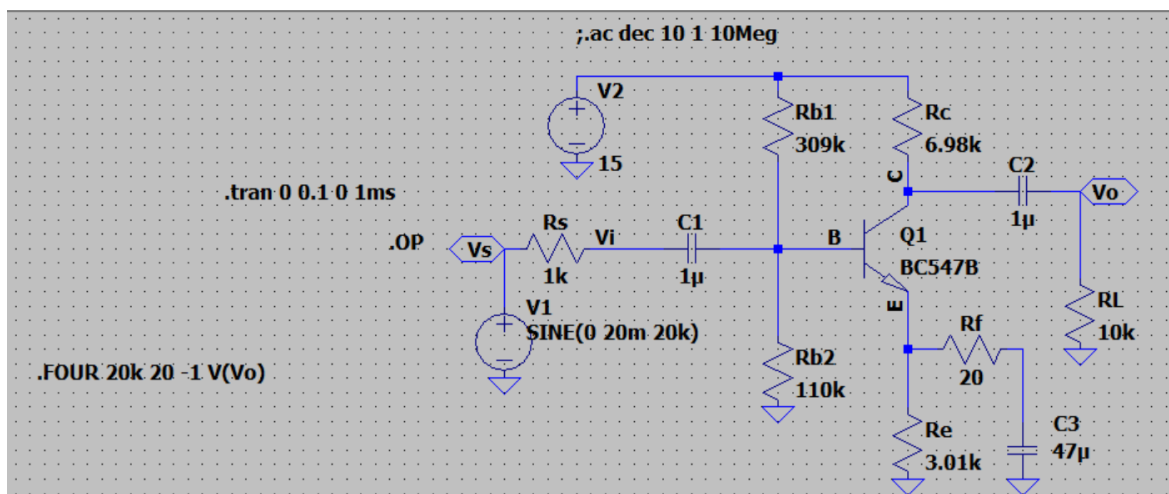


Fig. 1 A CE stage

Solution:

- (1) For $R_f = 0 \Omega$, $A_{v_simulated} = 127.6$ --(42 dB); $f_L = 127$ Hz; $f_H = 543$ KHz; THD = 10.6%
- (2) For $R_f = 20 \Omega$, $A_{v_simulated} = 78.5$ --(37.9 dB); $f_L = 78.1$ Hz; $f_H = 865$ KHz; THD = 4.45%
- (3) Disadvantage: gain A_v is dropped. Advantages: frequency bandwidth becomes wider; harmonic distortion becomes smaller.