

Literature:

Diode: p 166 – 172, 183-184, 197-210

Assignments:

2.1:

A logic circuit is shown in Fig. 1. The voltage drops of the diodes connected to A and B are 0.7 V and the voltage drop of the LED is 2 V.

- When A is connected to 0 V and B to 0 V, is the LED on or off? Why?
- When A is connected to 0 V and B to 5 V, is the LED on or off? Why?
- When A is connected to 5 V and B to 0 V, is the LED on or off? Why?
- When A is connected to 5 V and B to 5 V, is the LED on or off? Why?
- What logic gate is it?

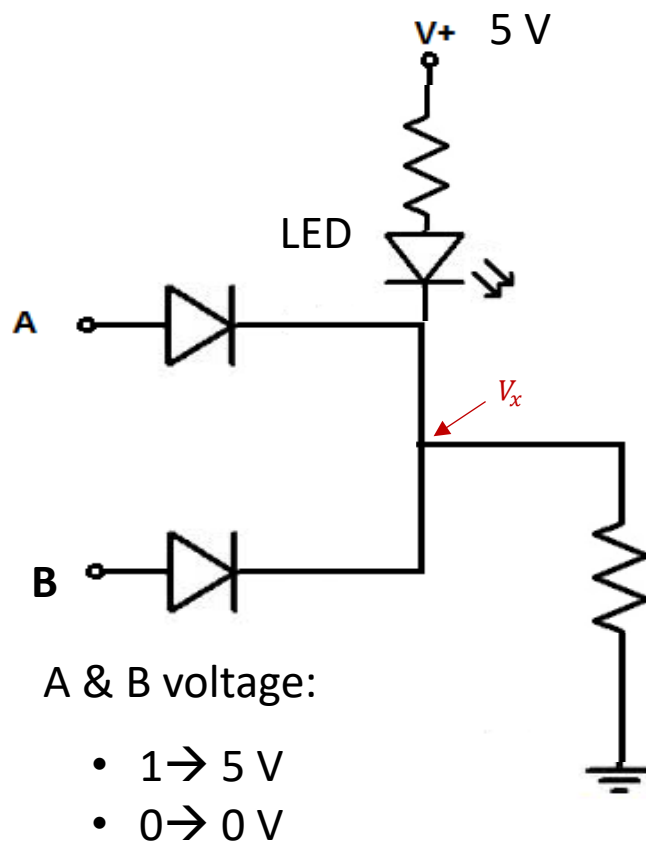


Fig. 1

### Solution:

- When  $A=0$  (0V) and  $B=0$ (0V)  $\Rightarrow$  diode A and B are off  $\Rightarrow$  The voltage across the LED  $> 2$  V  $\Rightarrow$  LED is on (1)
- When  $A=0$  (0V) and  $B=1$ (5V)  $\Rightarrow$  diode A is off, but diode B is on  $\Rightarrow V_x = 5-0.7 = 4.3$  V  $\Rightarrow$  The voltage across the LED  $= 5 - V_x = 0.7$  V  $< 2$  V  $\Rightarrow$  LED is off (0)
- When  $A=1$  (5V) and  $B=0$ (0V)  $\Rightarrow$  diode A is on, and diode B is off  $\Rightarrow V_x = 5-0.7 = 4.3$  V  $\Rightarrow$  The voltage across the LED  $= 5 - V_x = 0.7$  V  $< 2$  V  $\Rightarrow$  LED is off (0)
- When  $A=1$  (5V) and  $B=1$ (5V)  $\Rightarrow$  diode A is on, and diode B is on  $\Rightarrow V_x = 5-0.7 = 4.3$  V  $\Rightarrow$  The voltage across the LED  $= 5 - V_x = 0.7$  V  $< 2$  V  $\Rightarrow$  LED is off (0)
- It is a **NOR** gate.

2.2:

Half-wave rectifier LT spice simulation:

$V_{in} = 4\sin(2\pi 50t)$  , diode 1N4007,  $R = 1\text{ K}\Omega$ , and  $C = 0.0001\text{ F}$

plot the voltage across the resistor for the following cases:

1. Half-wave rectifier with a resistor R.
2. Half-wave rectifier with a capacitor C.
3. Half-wave rectifier with a capacitor C and a resistor R.
4. Half-wave rectifier with a capacitor C and a resistor R.

Change the capacitance of the capacitor to make the output signal smoother.

**Solution for 4:** We need to pick the type of the diode to 1N4007 in this simulation.

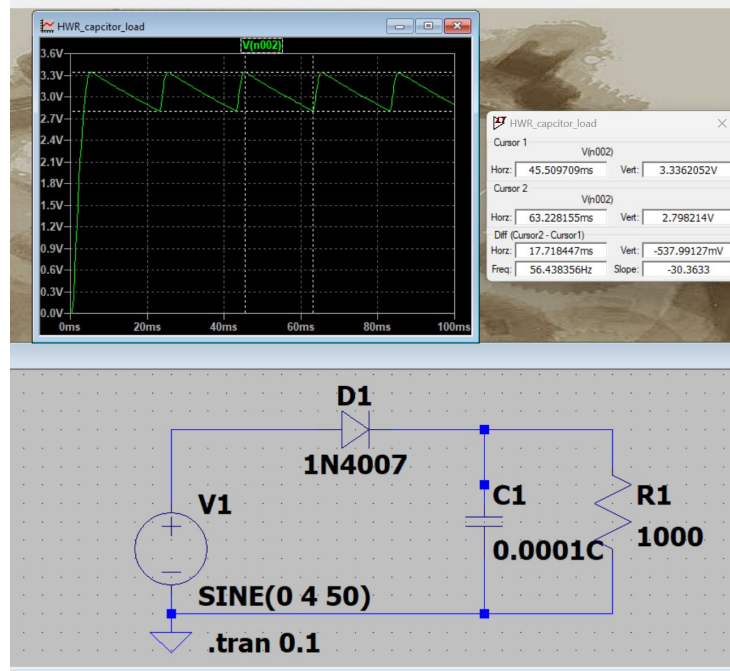


Fig 2.  $C = 0.0001$  F, the ripple amplitude of the output signal is around 0.5 V

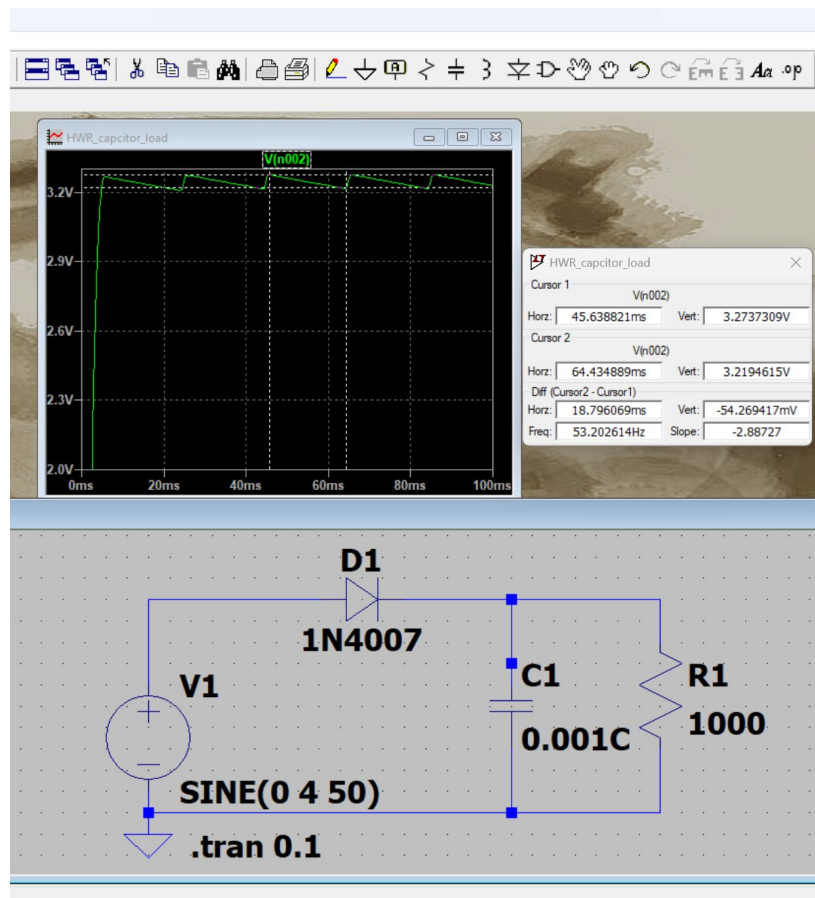


Fig 3. Increasing  $C = 0.001$  F, the ripple amplitude of the output signal is reduced to around 0.05 V

2.3:

Full-wave rectifier LT spice simulation:

$V_{in} = 4\sin(2\pi 50t)$ , diode 1N4007,  $R = 1\text{ K}\Omega$ , and  $C = 0.0001\text{ F}$

plot the voltage across the resistor for the following cases:

1. Full-wave rectifier with a resistor R.
2. Full-wave rectifier with a capacitor C.
3. Full-wave rectifier with a capacitor C and a resistor R.
4. Full-wave rectifier with a capacitor C and a resistor R.

Change the capacitance of the capacitor, i.e., change the value of C, to make the output signal smoother.

**Solution for 4:** We need to pick the type of the diode to 1N4007 in this simulation.

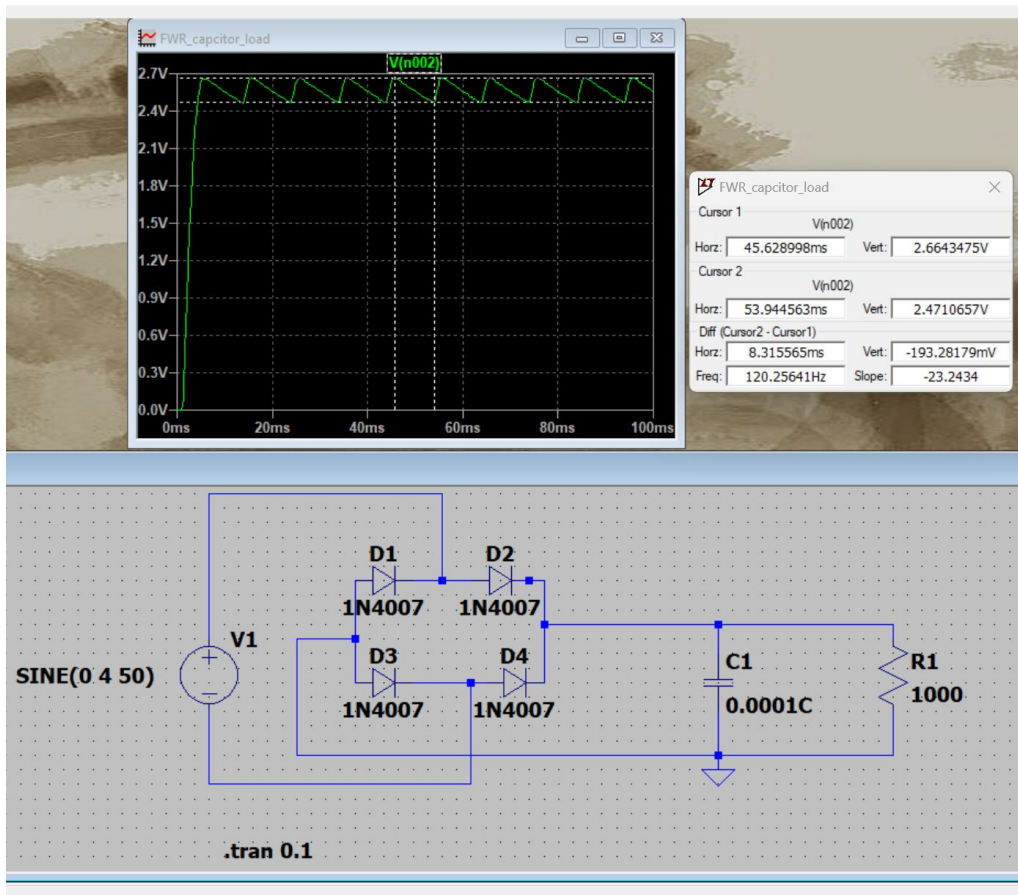


Fig 4.  $C = 0.0001\text{ F}$ , the ripple amplitude of the output signal is around 0.2 V, which is around the half of that of the half-wave rectifier in Fig. 2.

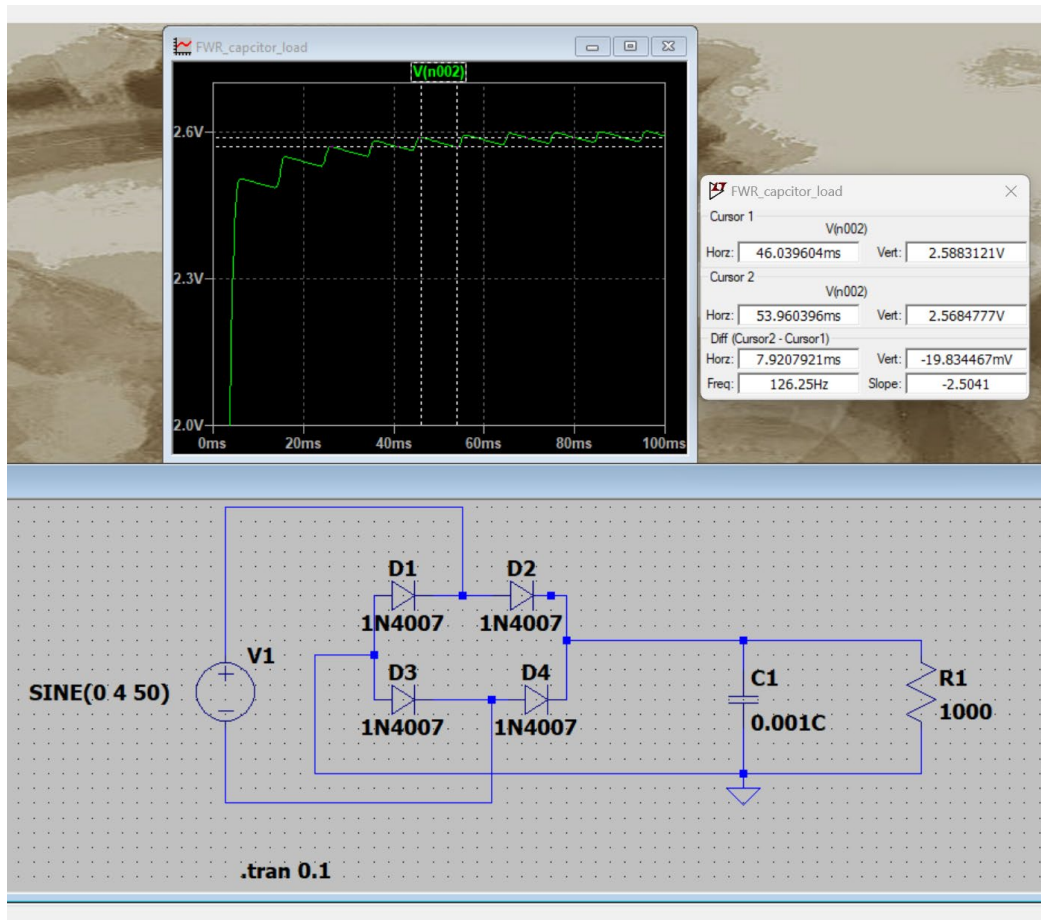


Fig 5. Increasing  $C = 0.001\text{ F}$ , the ripple amplitude of the output signal is reduced to around 0.02 V.