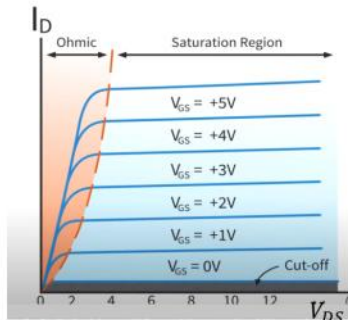


Operation regions of MOSFET



MOSFET transconductance parameter:

$$k_n = \mu_n C_{ox} W/L$$

- μ_n : mobility of the electrons at the surface of the channel
- C_{ox} : oxide capacitance
- W & L : width & length of the channel

Overdrive voltage: $V_{ov} = V_{GS} - V_{TH}$

Threshold voltage: $V_{TH} \sim 0.3 \text{ V} \sim 1 \text{ V}$

$$I_D = \begin{cases} 0, & \text{cut-off: } V_{GS} < V_{TH} \\ k_n[(V_{GS} - V_{TH})V_{DS} - \frac{1}{2}V_{DS}^2], & \text{triode: } V_{GD} > V_{TH} \\ \frac{1}{2}k_n(V_{GS} - V_{TH})^2(1 + \lambda V_{DS}), & \text{saturation: } V_{GD} < V_{TH} \end{cases}$$

cut-off: $V_{GS} < V_{TH}$


Triode and cut-off region: switching devices

triode: $V_{GD} > V_{TH}$


saturation: $V_{GD} < V_{TH}$

Saturation region: amplifier


High-frequency models of BJT and MOSFET

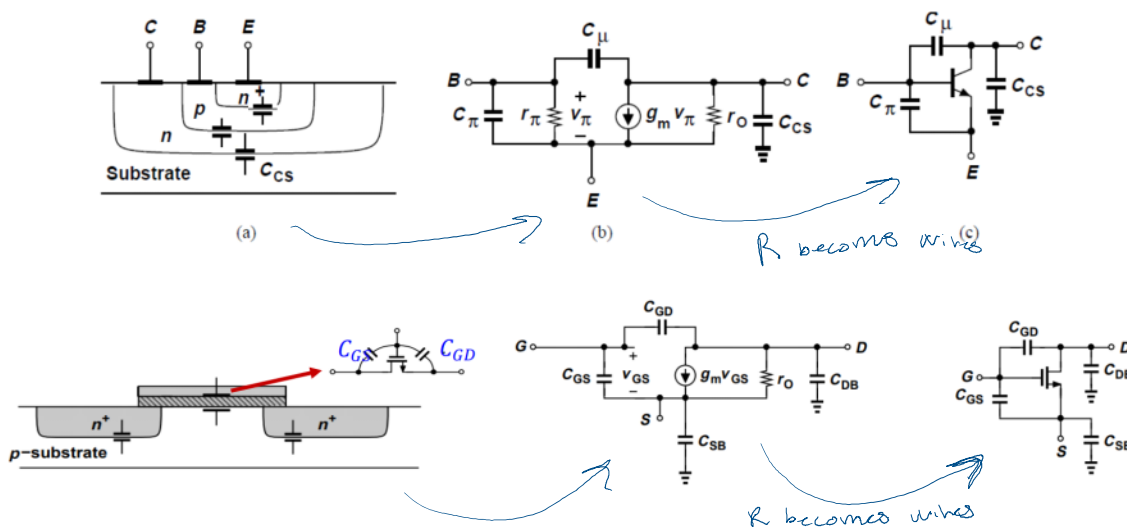

CE/CS frequency response

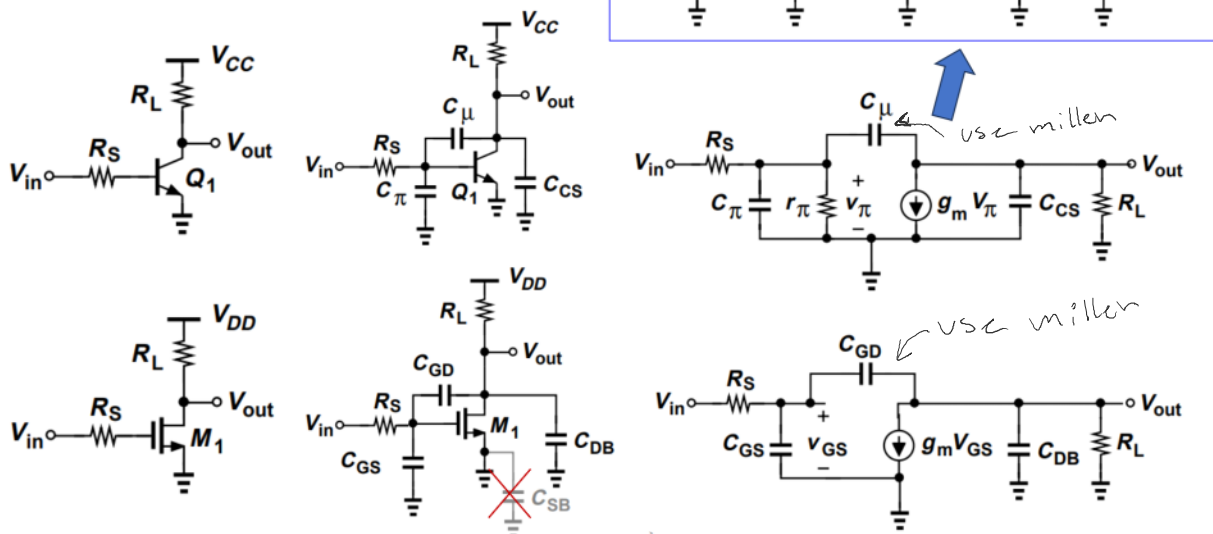

Approach I: finding poles by inspection

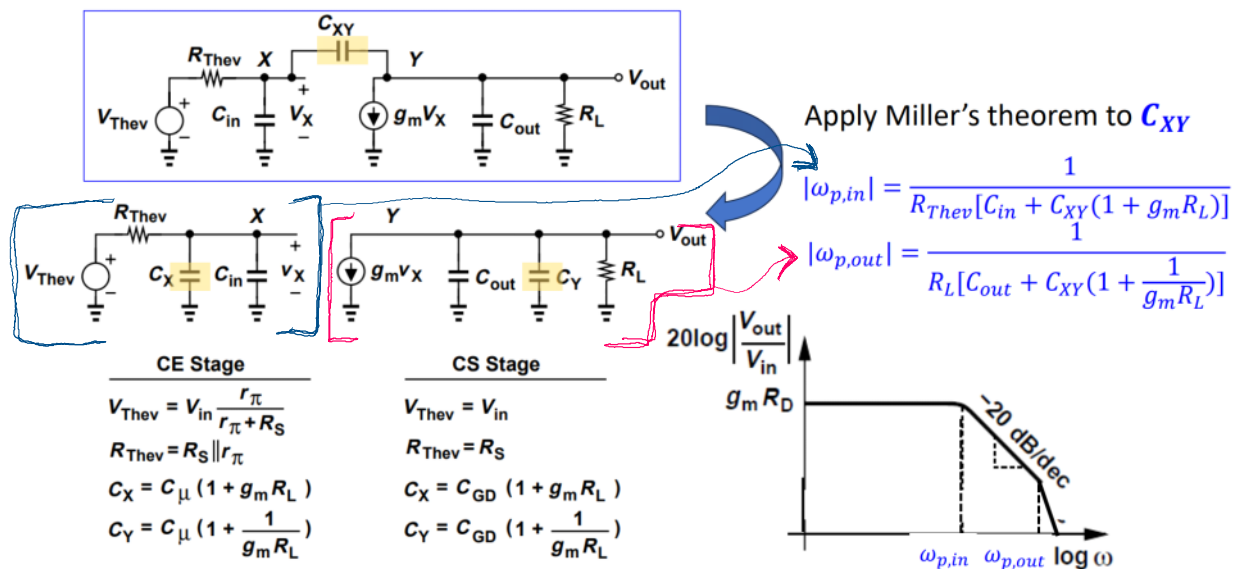

OR

$$C_{in, Miller} = C_f (1 - A_v)$$

$$C_{out, Miller} = C_f (1 - \frac{1}{A_v})$$

check maple doc

Low-frequency response-BJT

$$\frac{V_o}{V_{sig}} = A_M \frac{s}{s+\omega_{p1}} \frac{s+\omega_z}{s+\omega_{pE}} \frac{s}{s+\omega_{p2}}$$

$$\omega_{p1} = \frac{1}{\tau_{c1}} = \frac{1}{C_{c1}(R_B || r_{\pi} + R_{sig})}$$

$$\omega_{pE} = \frac{1}{\tau_{cE}} = \frac{1}{C_E [R_E || (\frac{1}{g_m} + \frac{R_B || R_{sig}}{\beta + 1})]}$$
 Dominant pole







$$\omega_{p2} = \frac{1}{\tau_{c2}} = \frac{1}{C_{c2}(R_D + R_L)}$$

$$\omega_z = \frac{1}{C_E R_E}$$


$$R_B = R_{B1} || R_{B2} \quad r_{\pi} = \frac{\beta}{g_m} = \beta r_e$$

Short-circuit time constant method:

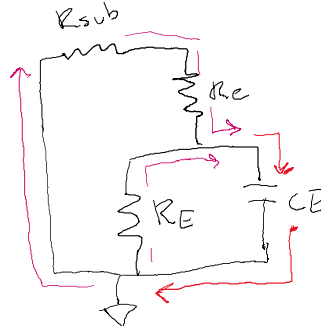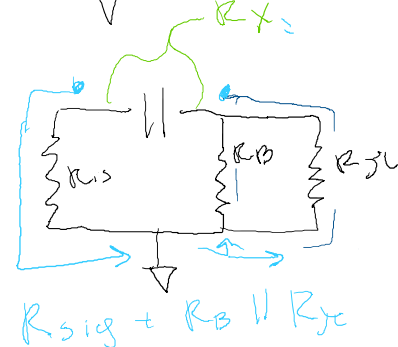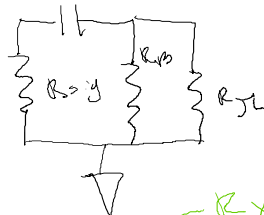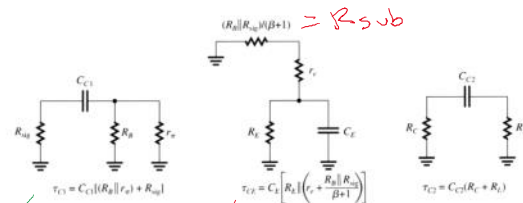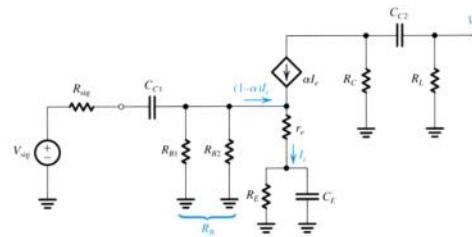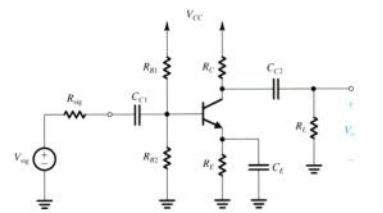- Short other capacitors
- turn off sources:
 - Voltage source \rightarrow short circuit
 - Current source \rightarrow open circuit




$$R_E || (R_{sub} + R_c)$$

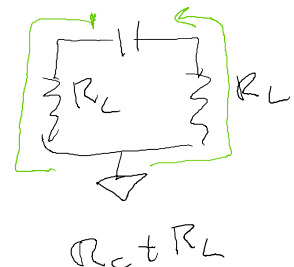

check maple doc

Low-frequency response--MOSFET

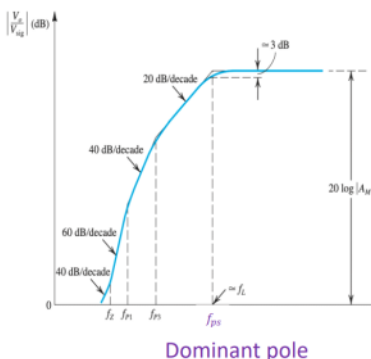

$$\frac{V_o}{V_{sig}} = A_M \frac{s}{s+\omega_{p1}} \frac{s+\omega_z}{s+\omega_{ps}} \frac{s}{s+\omega_{p2}}$$




$$\omega_{p1} = \frac{1}{\tau_{c1}} = \frac{1}{C_{c1}(R_G + R_{sig})}$$


$$\omega_{ps} = \frac{1}{\tau_{cs}} = \frac{1}{C_s(R_S || \frac{1}{g_m})}$$

$$\omega_{p2} = \frac{1}{\tau_{c2}} = \frac{1}{C_{c2}(R_D + R_L)}$$

$$\omega_z = \frac{1}{C_S R_S}$$

$$R_G = R_{G1} || R_{G2}$$

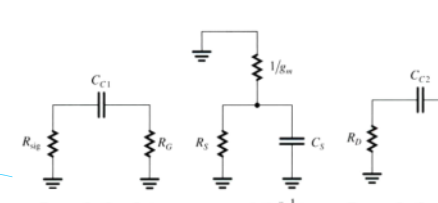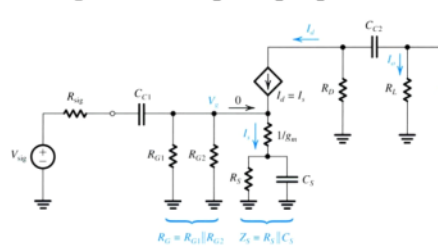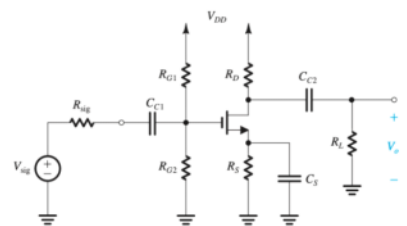

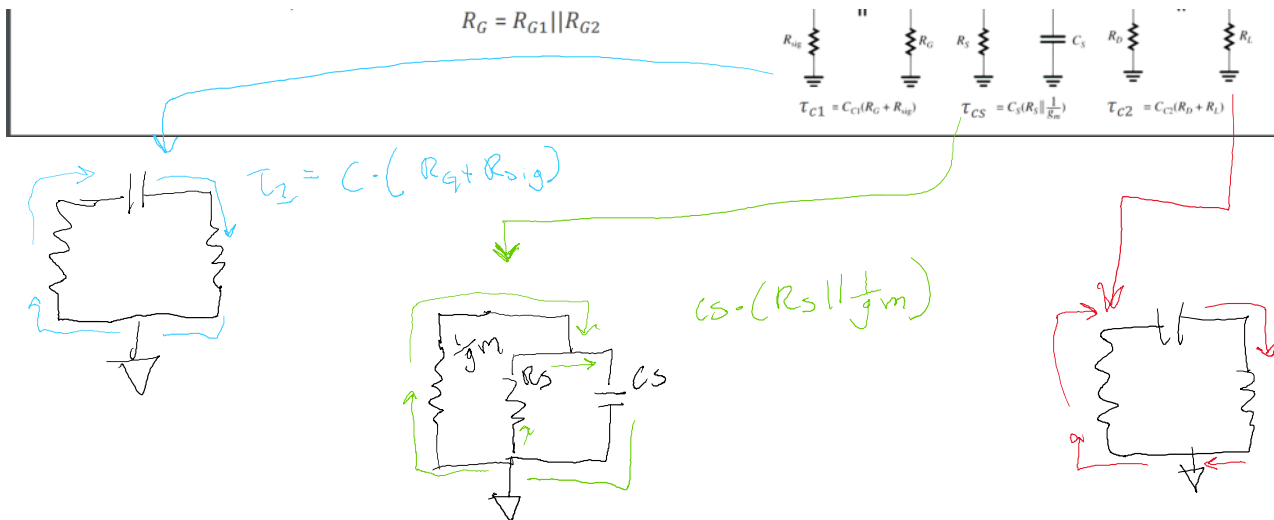


Low frequency design

- Design the C_{C1} , C_{CE} and C_{C2} to achieve a given f_L

$$f_{C1} = f_{C2} = 0.1 f_L$$


$$f_{CE} = 0.8 f_L$$

- $\omega_{p1} = 2\pi f_{C1} = \frac{1}{C_{C1}(R_B || r_{\pi} + R_{sig})}$
- $\omega_{pE} = 2\pi f_{CE} = \frac{1}{C_E[R_E || (\frac{1}{g_m} + \frac{R_B || R_{sig}}{\beta + 1})]}$
- $\omega_{p2} = 2\pi f_{C2} = \frac{1}{C_{C2}(R_D + R_L)}$

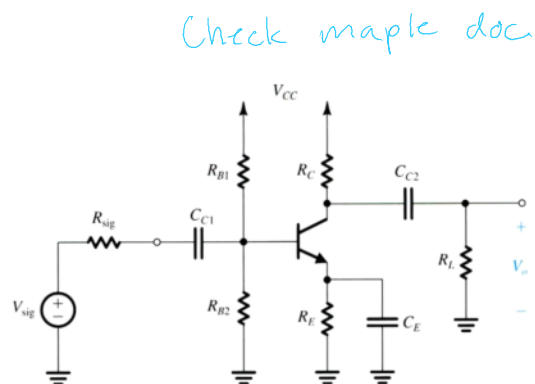


Nonlinear system

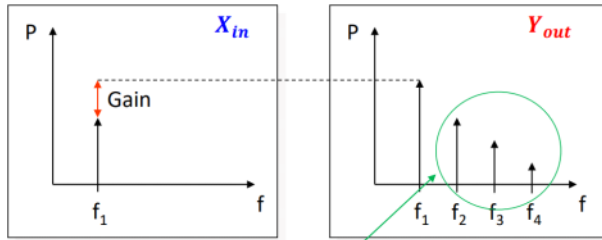- $Y_{out} = f(X_{in})$: nonlinear function
 - X and Y could be V or I
 - $Y_{out} = \alpha_1 X_{in} + \alpha_2 X_{in}^2, Y_{out} = e^{\frac{X_{in}}{a}} \dots$
 - Capacitors, diodes, transistor



Undesirable frequency components

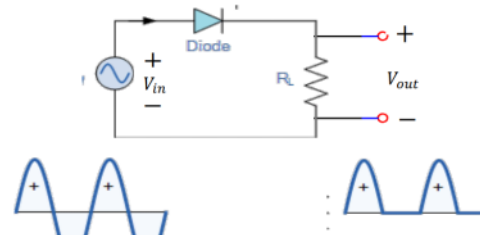

General nonlinear system

$$Y_{out} = f(X_{in}) = f(a) + f'(a)(X_{in} - a) + \frac{f''(a)}{2!}(X_{in} - a)^2 + \dots$$

$$X_{in} = X_{in,Q} + x_{in}$$

In small-signal model, assume x_{in} is a sin wave centered at $a = 0$

$$\begin{aligned} Y_{out} &= f(0) + f'(0)x_{in} + \frac{f''(0)}{2!}x_{in}^2 + \frac{f'''(0)}{3!}x_{in}^3 + \dots \\ &= \alpha_0 + \alpha_1 x_{in} + \alpha_2 x_{in}^2 + \alpha_3 x_{in}^3 + \dots \end{aligned}$$

General nonlinear system

$$Y_{out} = \alpha_0 + \alpha_1 x_{in} + \alpha_2 x_{in}^2 + \alpha_3 x_{in}^3 + \dots$$

- $x_{in} = A \cos(\omega t)$
- $x_{in}^2 = A^2 \cos^2(\omega t) = A^2 \frac{1 + \cos(2\omega t)}{2}$
- $x_{in}^3 = A^3 \cos^3(\omega t) = A^3 \frac{3\cos(\omega t) + \cos(3\omega t)}{4}$

Total harmonic distortion (THD):

$$THD = \sqrt{HD_2^2 + HD_3^2 + HD_4^2 + \dots}$$

DC:

$$\beta_0 = \alpha_0 + \alpha_2 \frac{A^2}{2}$$

2nd Harmonic:

$$\beta_2 = \alpha_2 \frac{A^2}{2}$$

Harmonic distortion (HD):

2nd Harmonic:

$$HD_2 = \frac{\beta_2}{\beta_1} \approx \frac{\alpha_2}{2\alpha_1} A$$

Fundamental:

$$\beta_1 = \alpha_1 A + \alpha_3 \frac{3A^3}{4} \approx \alpha_1 A$$

3rd Harmonic:


$$\beta_3 = \alpha_3 \frac{A^3}{4}$$

3rd Harmonic:

$$HD_3 = \frac{\beta_3}{\beta_1} \approx \frac{\alpha_3}{4\alpha_1} A^2$$

Example for harmonic distortion calculation

Here $\beta \approx$ "height"

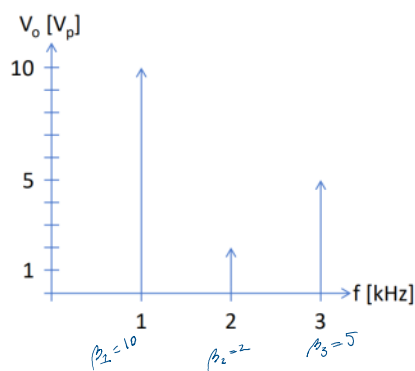


$$HD_2 = \frac{\beta_2}{\beta_1} = \frac{2}{10} = 0.2 \rightarrow 20\%$$

$$HD_3 = \frac{\beta_3}{\beta_1} = \frac{5}{10} = 0.5 \rightarrow 50\%$$

$$THD = \sqrt{HD_2^2 + HD_3^2} = \sqrt{0.2^2 + 0.5^2} = 0.54 \rightarrow 54\%$$

Nonlinear system example--BJT

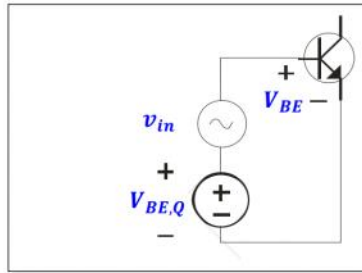

Taylor series expansion:

$$e^{x/a} = 1 + \frac{1}{a}x + \frac{1}{2!a^2}x^2 + \dots + \frac{1}{n!a^n}x^n + \dots$$

$$\begin{aligned} I_C &= I_S e^{V_{BE}/V_T} = I_S e^{(V_{BE,Q} + v_{in})/V_T} = I_S e^{V_{BE,Q}/V_T} e^{v_{in}/V_T} = I_{CQ} e^{v_{in}/V_T} \\ &= I_{CQ} \left(1 + \frac{1}{V_T} v_{in} + \frac{1}{2! V_T^2} v_{in}^2 + \frac{1}{3! V_T^3} v_{in}^3 + \dots \right) \\ &= I_{CQ} + \frac{I_{CQ}}{V_T} v_{in} + \frac{I_{CQ}}{2! V_T^2} v_{in}^2 + \frac{I_{CQ}}{3! V_T^3} v_{in}^3 + \dots \\ &= \alpha_0 + \alpha_1 v_{in} + \alpha_2 v_{in}^2 + \alpha_3 v_{in}^3 + \dots \end{aligned}$$

DC:

$$\beta_0 = \alpha_0 + \alpha_2 \frac{A^2}{2}$$

2nd Harmonic:

$$\beta_2 = \alpha_2 \frac{A^2}{2}$$

Fundamental:

$$\beta_1 = \alpha_1 A + \alpha_3 \frac{3A^3}{4} \approx \alpha_1 A$$


3rd Harmonic:

$$\beta_3 = \alpha_3 \frac{A^3}{4}$$

Total harmonic distortion (THD):

$$\begin{aligned} THD &= \sqrt{HD_2^2 + HD_3^2 + HD_4^2 + \dots} \\ &= \sqrt{\left(\frac{\beta_2}{\beta_1}\right)^2 + \left(\frac{\beta_3}{\beta_1}\right)^2 + \left(\frac{\beta_4}{\beta_1}\right)^2 + \dots} \end{aligned}$$

Nonlinear system example--MOSFET

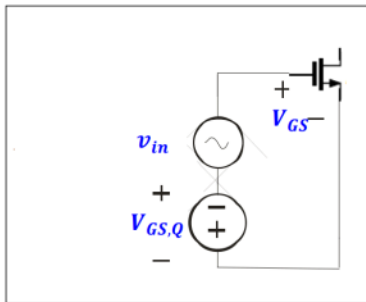

$$\begin{aligned} I_D &= \frac{1}{2} k_n (V_{GS} - V_{TH})^2 = \frac{1}{2} k_n (V_{GS,Q} - V_{TH} + v_{in})^2 \\ &= \frac{1}{2} k_n (V_{GS,Q} - V_{TH})^2 \left(1 + \frac{v_{in}}{V_{GS,Q} - V_{TH}} \right)^2 \\ &= I_{DQ} \left(1 + \frac{2}{V_{GS,Q} - V_{TH}} v_{in} + \frac{1}{(V_{GS,Q} - V_{TH})^2} v_{in}^2 \right) \\ &= I_{DQ} + \frac{2I_{DQ}}{V_{GS,Q} - V_{TH}} v_{in} + \frac{I_{DQ}}{(V_{GS,Q} - V_{TH})^2} v_{in}^2 \\ &= \alpha_0 + \alpha_1 v_{in} + \alpha_2 v_{in}^2 \end{aligned}$$

DC:

$$\beta_0 = \alpha_0 + \alpha_2 \frac{A^2}{2}$$

2nd Harmonic:

$$\beta_2 = \alpha_2 \frac{A^2}{2}$$

Fundamental:

$$\beta_1 = \alpha_1 A$$

3rd Harmonic:



$$\beta_3 = 0$$

Total harmonic distortion (THD):

$$\begin{aligned} THD &= \sqrt{HD_2^2 + HD_3^2 + HD_4^2 + \dots} \\ &= \frac{\beta_2}{\beta_1} = HD_2 \end{aligned}$$

Design consideration

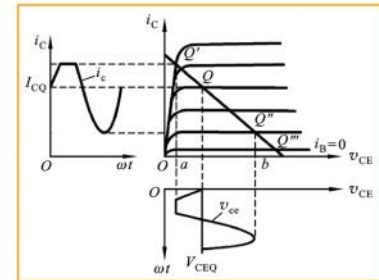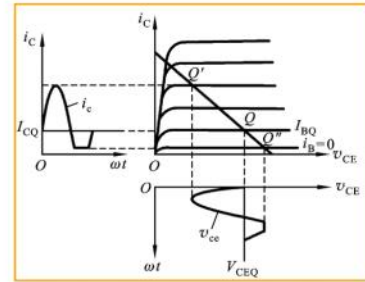- Properly bias
 - BJT
 - Active forward region $\rightarrow V_{BE} \geq 0.7 \text{ V} \text{ \& } V_{CE} \geq V_{BE}$
 - MOSFET
 - Saturation $\rightarrow V_{DS} > V_{GS} - V_{TH}$
- Select suitable Q point (clip distortion)
- Small-signal assumption
 - BJT
 - Small-signal assumption $\rightarrow v_{in} < 0.2 V_T$
 - MOSFET
 - Small-signal assumption $\rightarrow v_{in} < 0.2 (V_{GS,Q} - V_{TH})$



Assignment

Assignments:

9.1:

Use the short-circuit time constant method to determine the capacitor values of C_1 , C_2 and C_3 , so that $f_L = 100 \text{ Hz}$ can be achieved for the circuit in Fig. 1. Where $g_m = 3.82 \cdot 10^{-2}$, $\beta = 301$.

Hint: $r_\pi = \beta/g_m$, $r_e = 1/g_m$.

- (1) C_1 , C_2 and $C_3 = ?$
- (2) Run the LTspice simulation to check your calculation by comparing with the simulated f_L .
- (3) Run the LTspice simulation to find the f_H .
- (4) Run the LTspice simulation to observe harmonic distortion.

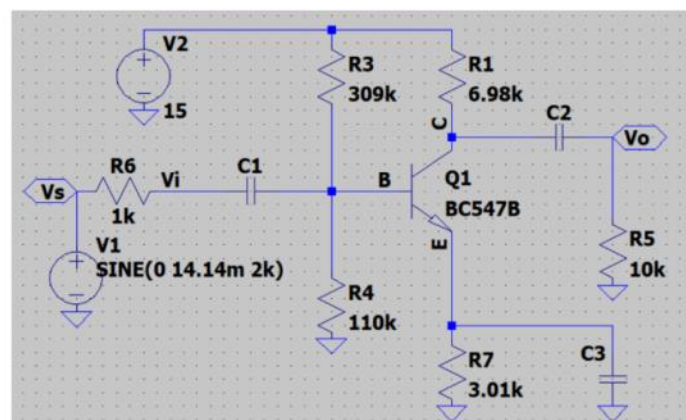


Fig. 1 A CE stage

Fig. 1 A CE stage

Solution:

(1)

$$f_{C_1} = f_{C_2} = 0.1f_L = 10 \text{ Hz}$$

$$f_{C_E} = 0.8f_L = 80 \text{ Hz}$$

$$r_\pi = \frac{\beta}{g_m} = 7.88 \text{ K}\Omega$$

$$R_B = R_3 || R_4 = 81.1 \text{ K}\Omega$$

$$R_E = R_7 = 3.01 \text{ K}\Omega$$

$$R_{C_1} = (R_B || r_\pi) + R_{sig} = 8.18 \text{ K}\Omega$$

$$R_{C_E} = R_E || \left(\frac{1}{g_m} + \frac{R_B || R_{sig}}{\beta + 1} \right) = 29.16 \Omega$$

$$R_{C_2} = R_C + R_L = R_1 + R_5 = 16.98 \text{ K}\Omega$$

$$2\pi f_{C_1} = \frac{1}{C_{C_1} R_{C_1}} \rightarrow C_{C_1} = \frac{1}{2\pi f_{C_1} R_{C_1}} = 1.94 \mu\text{F}$$

$$2\pi f_{C_E} = \frac{1}{C_{C_E} R_{C_E}} \rightarrow C_{C_E} = \frac{1}{2\pi f_{C_E} R_{C_E}} = 68.2 \mu\text{F}$$

$$2\pi f_{C_2} = \frac{1}{C_{C_2} R_{C_2}} \rightarrow C_{C_2} = \frac{1}{2\pi f_{C_2} R_{C_2}} = 0.94 \mu\text{F}$$

Check:
classic BJT Design.mw
(maple doc)
for how to do this.