

Blackboard Notes for lecture - 4

slide 4:

the slope of the straight line will contribute to different α point.

slide 7:

the α point should be properly selected, otherwise, it will result in waveform distortion.

slide 8:

$$A_v = - \frac{\beta \cdot R_c \cdot R_L}{r_{\pi}(R_c + R_L)}, \text{ be aware of the minus sign here,}$$

it means the ~~phase~~ output signal and input signal are out of phase (180° phase difference).

the amplification coefficient can be tuned by adjusting the values of R_c and R_L .

slide 9:

please be aware of i_i which is generally not equal to i_B . calculate input impedance and output impedance according to definitions.

slide 17;

for any complicated BJT circuit:

You need to formulate v_i and v_o , then

calculate $A_v = \frac{v_o}{v_i}$

Also, DC circuit should be first drawn to determine Q point.

then AC circuit should be built to formulate v_i and v_o .