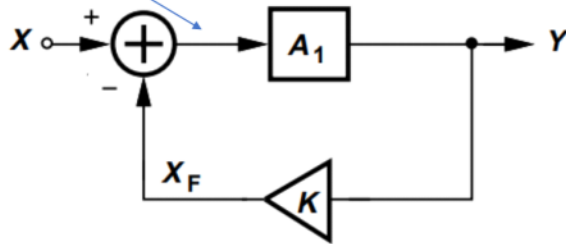


Transfer function of closed-loop system

Error signal = $X - X_F$




$$A_{CL} = \frac{Y}{X} = \frac{A_1}{1 + KA_1} \text{ --- closed-loop gain}$$

A_1 is the open-loop gain
 K is the feedback factor

$$KA_1 > 0 \rightarrow |A_{CL}| < |A_1|$$

Example

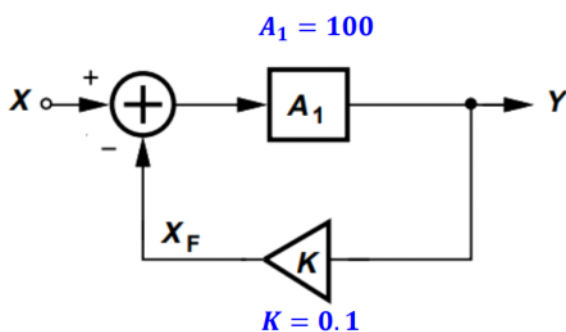

Nominal gain of an amp: $A_1 = 100$
 Actual gain in application: $A'_1 = 50$


How much does A_1 change?
 How much does the closed-loop gain A_{CL} change?

$$A_{CL} = A_1 / (1 + KA_1) = 100/11 = 9.09$$

$$A_{CL}' = A'_1 / (1 + KA'_1) = 50/6 = 8.33$$

A_{CL} change: 8.3%

Feedback system example

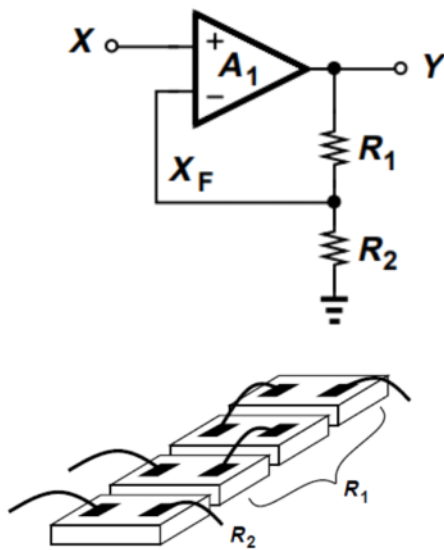

The op amp A1 performs two functions:

- subtraction
- Amplification


What is the closed-loop gain?

$$A_{cl} = \frac{Y}{X} = \frac{A_1}{1 + KA_1} = \frac{A_1}{1 + \frac{R_2}{R_1 + R_2} A_1}$$

$$A_{cl} \approx \frac{R_1 + R_2}{R_2} = 1 + \frac{R_1}{R_2}, \text{ if } \frac{R_2}{R_1 + R_2} A_1 \gg 1$$

Loop-gain


- Open-loop gain: A_1
- Closed-loop gain: $A_{cl} = \frac{Y}{X} = \frac{A_1}{1 + KA_1}$
- Loop-gain: KA_1
 - Procedure to measure loop-gain
 - Set the input X to zero (X is voltage \rightarrow AC ground; if X is current \rightarrow open)
 - Break the loop at an arbitrary point
 - Apply a test signal V_{test} at one terminal and measure the signal V_F at the other terminal
 - Calculate the loop-gain $-\frac{V_F}{V_{test}} = KA_1$
 - $\frac{V_F}{V_{test}} < 0 \rightarrow$ negative feedback
 - $\frac{V_F}{V_{test}} > 0 \rightarrow$ positive feedback

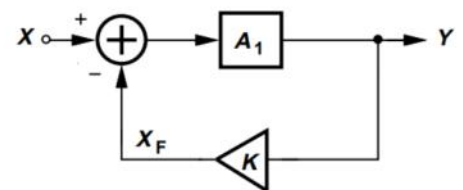

Summary of negative feedback concept

- Sacrifice the open-loop gain A_1 to benefit from negative feedback
- The feedback signal X_F is a good copy of input signal X
- The feedback factor K is normally independent to frequency
 - Make Y a good (scaled by $1/K$) copy of X
 - Wider frequency band
 - Better linearity
- If loop-gain $KA_1 \gg 1 \Rightarrow A_{CL} \approx \frac{1}{K}$, relatively independent of A_1
 - Factors that cause A_1 to vary have less impact on the closed-loop gain
 - Factors: temperature, supply voltage, frequency, load impedance

Gain desensitization example

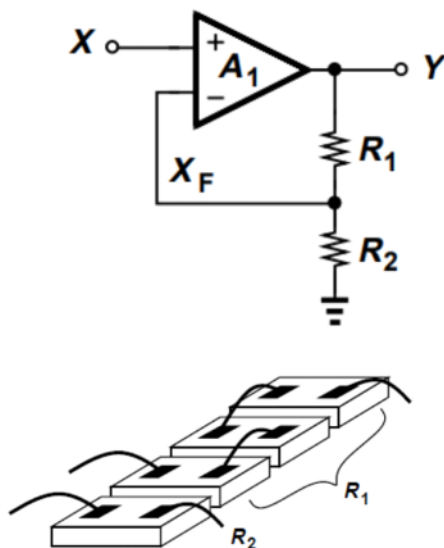


Assume the nominal gain of $A_1=100$ and $\frac{R_1}{R_2} = 3$. Due to e.g., temperature, supply voltage, frequency and loading impedance, A_1 drops to 50.

- How does the closed-loop gain A_{CL} change?

$$A_{CL} = \frac{Y}{X} = \frac{A_1}{1 + KA_1} = \frac{A_1}{1 + \frac{R_2}{R_1 + R_2} A_1}$$

Linearity improvement

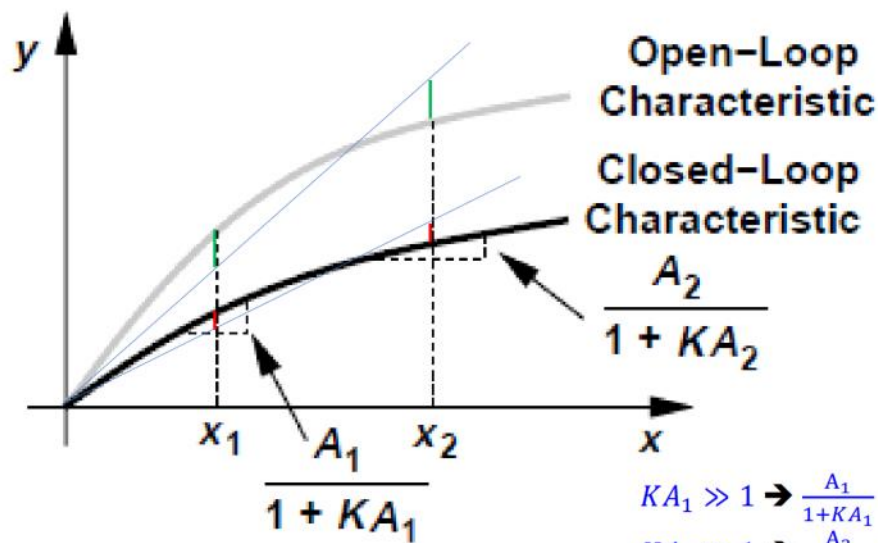


$$KA_1 \gg 1 \rightarrow \frac{A_1}{1+KA_1} \approx K, \text{ when } KA_1 \gg 1$$

$$KA_2 \gg 1 \rightarrow \frac{A_2}{1+KA_2} \approx K, \text{ when } KA_2 \gg 1$$

Modification of input and output impedance

Voltage-voltage FB

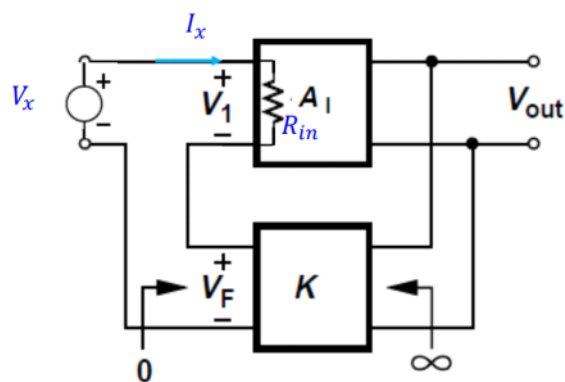

$$V_1 = I_x R_{in}$$


$$V_{out} = A_1 I_x R_{in}$$

$$V_F = K A_1 I_x R_{in}$$

$$V_x = V_1 + V_F$$

$$\rightarrow R_{in,CL} = V_x / I_x = R_{in}(1 + KA_1)$$

A better voltage sensor

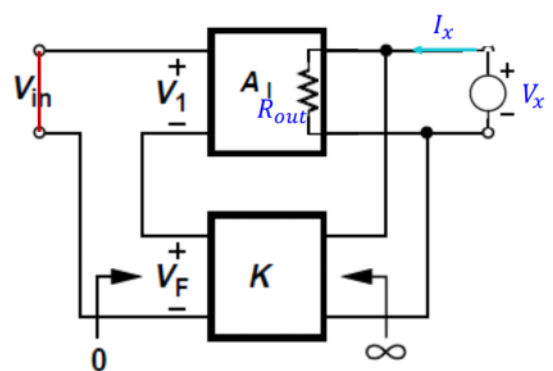


$$V_x = I_x R_{out}$$

$$V_1 = -V_F = -K V_x$$

$$\rightarrow R_{out,CL} = V_x / I_x = R_{out} / (1 + KA_1)$$

A better voltage source

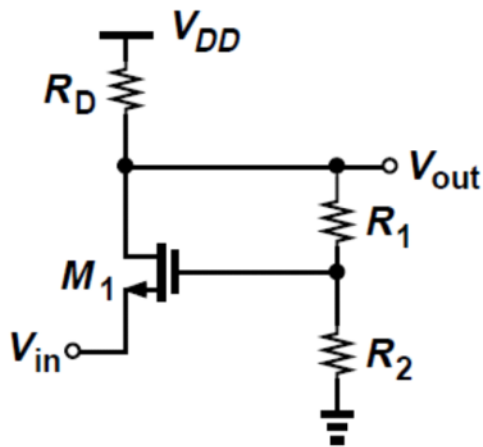Modification of input and output impedance



Assume $R_1 + R_2 \gg R_D$

$$A_1 = g_m R_D$$

$$K = \frac{R_2}{R_1 + R_2}$$

$$A_{CL} = \frac{A_1}{1 + KA_1}$$


$$R_{in} = 1/g_m$$

$$R_{out} = R_D$$

$$R_{in,CL} = R_{in}(1 + KA_1)$$


$$R_{out,CL} = R_{out}/(1 + KA_1)$$

Feedback topologies

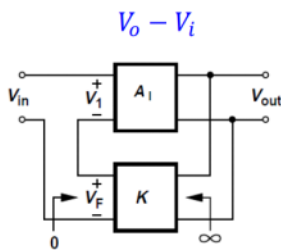


$$R_{in,CL} = R_{in}(1 + KA_1)$$

$$R_{out,CL} = R_{out}/(1 + KA_1)$$

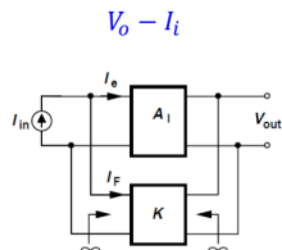


$$R_{in,CL} = R_{in}/(1 + KA_1)$$

$$R_{out,CL} = R_{out}/(1 + KA_1)$$

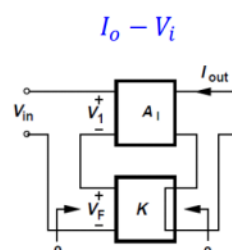

$$R_{in,CL} = R_{in}(1 + KA_1)$$





$$R_{out,CL} = R_{out}(1 + KA_1)$$

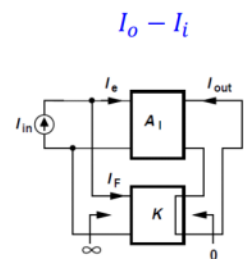

$$R_{in,CL} = R_{in}/(1 + KA_1)$$

$$R_{out,CL} = R_{out}(1 + KA_1)$$

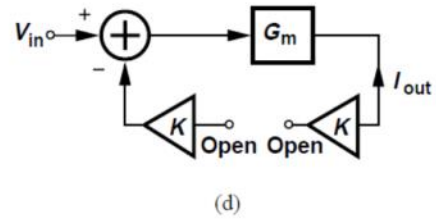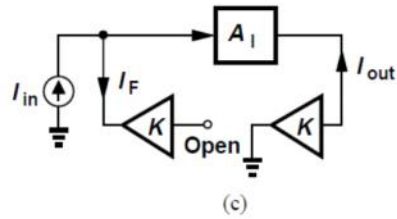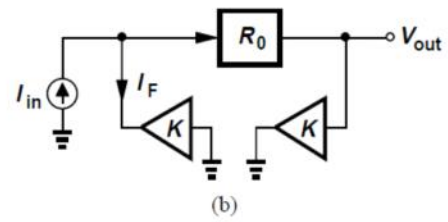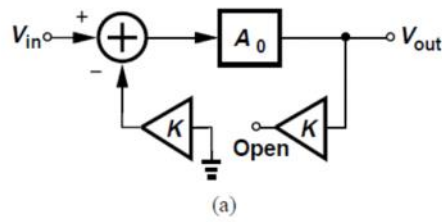Rules for breaking the feedback network(self-study)



Assignments:

10.1:

A CE stage circuit without (by setting $R_f = 0$) or with feedback (by setting $R_f = 20\ \Omega$) is shown in Fig. 1.

- (1) Set $R_f = 0$, i.e., without negative feedback, run the simulation and find out $A_v = ?$
 $f_L = ?$ $f_H = ?$ THD = ? @ 20KHz.
- (2) Set $R_f = 20$, i.e., with negative feedback, run the simulation and find out $A_v = ?$
 $f_L = ?$ $f_H = ?$ THD = ? @ 20KHz.
- (3) Comparing the results obtained in (1) and (2), discuss what is the advantages and disadvantages by introducing negative feedback into the circuit.

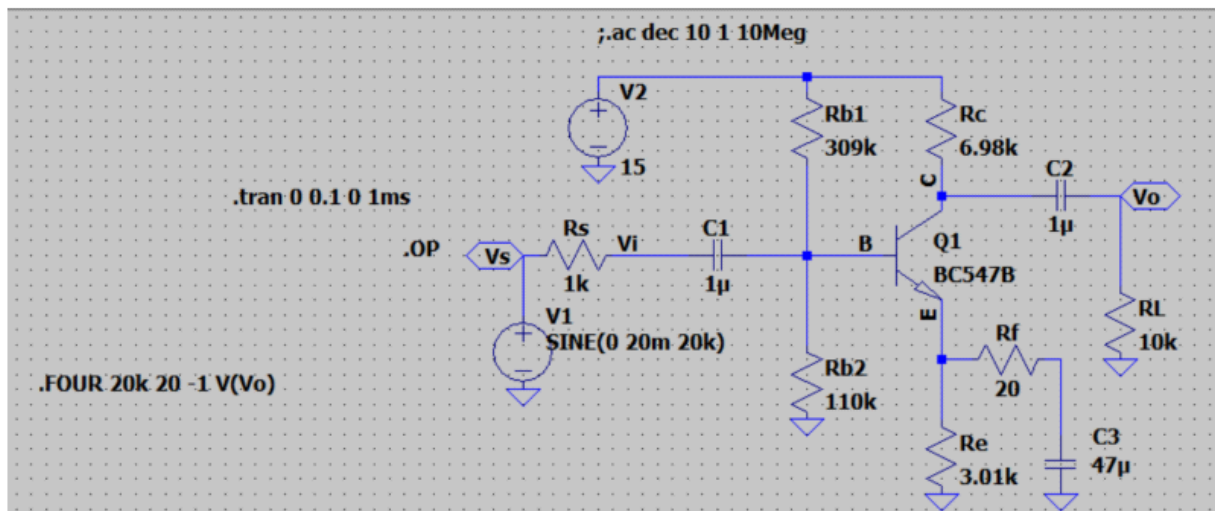


Fig. 1 A CE stage

Solution:

- (1) For $R_f = 0\ \Omega$, $A_{v_simulated} = 127.6$ --(42 dB); $f_L = 127\ \text{Hz}$; $f_H = 543\ \text{KHz}$; THD = 10.6%
- (2) For $R_f = 20\ \Omega$, $A_{v_simulated} = 78.5$ --(37.9 dB); $f_L = 78.1\ \text{Hz}$; $f_H = 865\ \text{KHz}$; THD = 4.45%
- (3) Disadvantage: gain A_v is dropped. Advantages: frequency bandwidth becomes wider; harmonic distortion becomes smaller.