
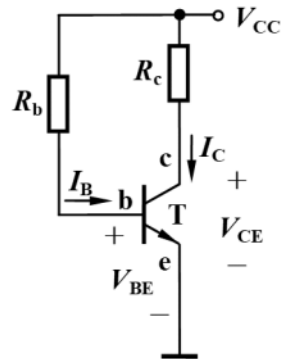


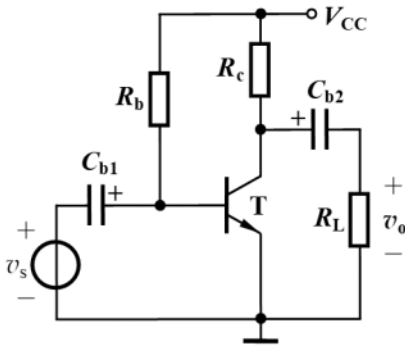

Using a diagram to analyze a BJT amplification circuit:

First step: draw the DC circuit



Input $i-v$ curve:



$$v_{BE} = V_{CC} - i_B R_b$$

Output $i-v$ curve:
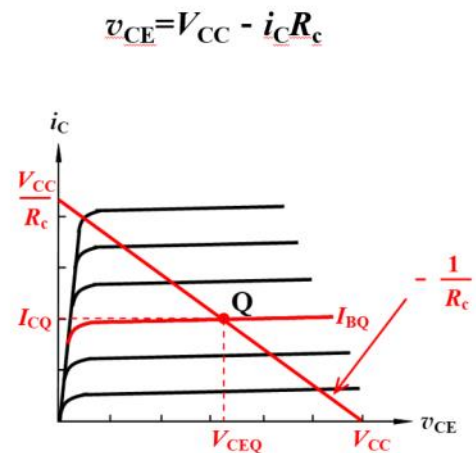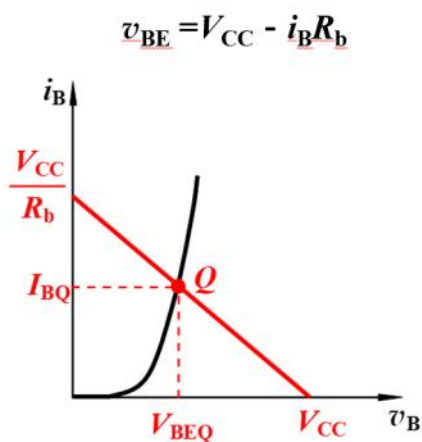
$$v_{CE} = V_{CC} - i_C R_c$$

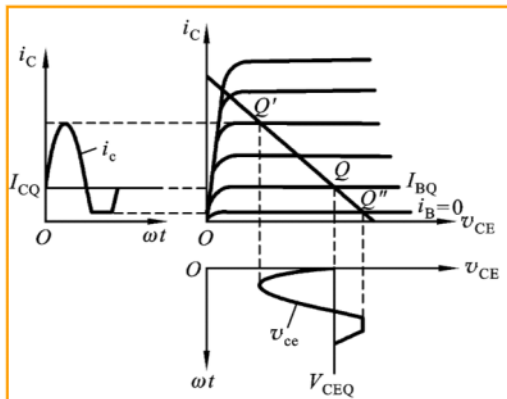


Diagram analysis of static operating point :






The effects of Q point on waveform distortion:





Cutoff distortion

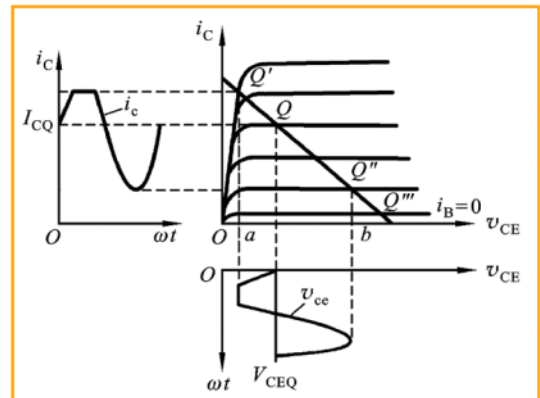


Saturation distortion




For the AC signal diagram:

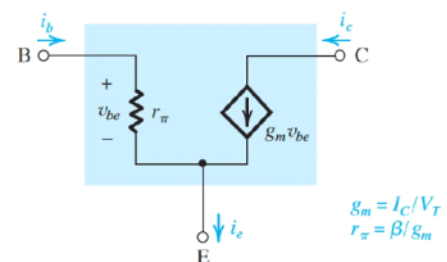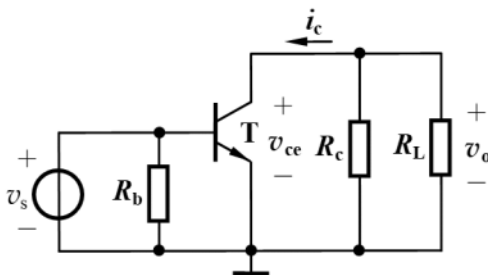

Small-signal model of a BJT

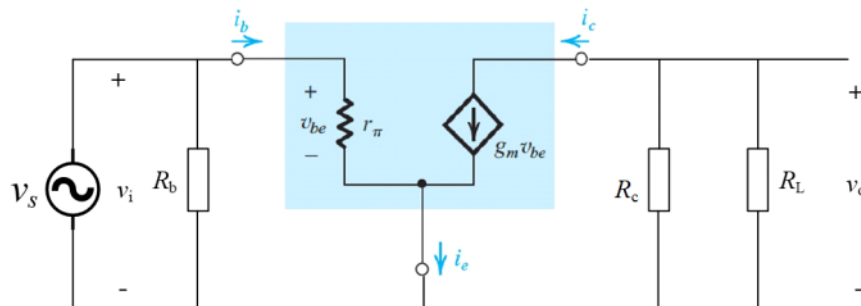

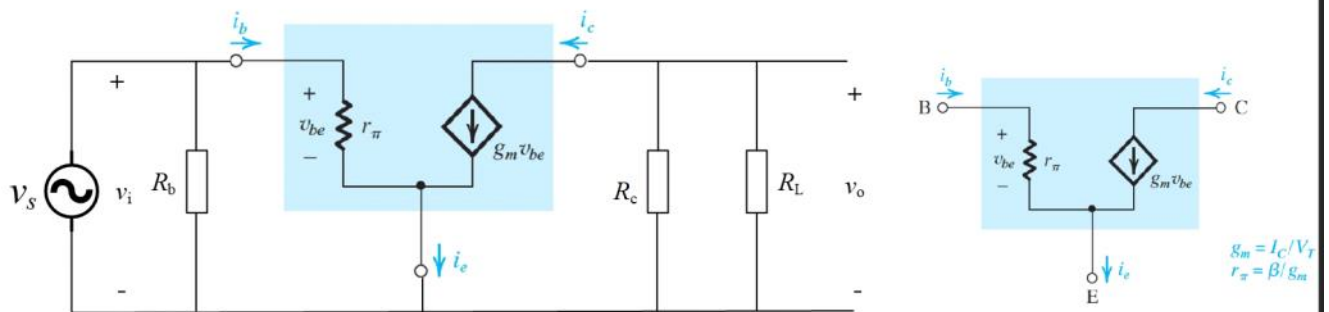

$$v_i = v_{be} = i_b r_\pi$$

$$i_c = g_m v_{be} = g_m i_b r_\pi = g_m i_b \beta / g_m \\ = \beta i_b$$


$$v_o = -i_c \cdot \left(\frac{R_c R_L}{R_c + R_L} \right)$$

AC small-signal amplification coefficient:

$$A_V = \frac{v_o}{v_i} = \frac{-i_c \cdot \left(\frac{R_c R_L}{R_c + R_L} \right)}{i_b r_\pi} = -\frac{\beta \cdot R_c R_L}{r_\pi (R_c + R_L)}$$




Input and output impedances:

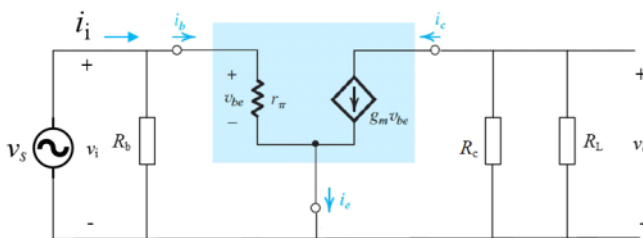

Input impedance:
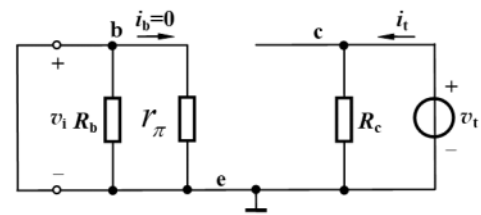
$$R_i = \frac{v_i}{i_i} = \frac{R_b r_\pi}{R_b + r_\pi}$$



Output impedance:


$$R_o = \left. \frac{v_t}{i_t} \right|_{v_s=0, R_L=\infty} = R_c$$

R_L is replaced with a voltage source (v_t):

Input source is short:



For a more complicated BJT circuit:

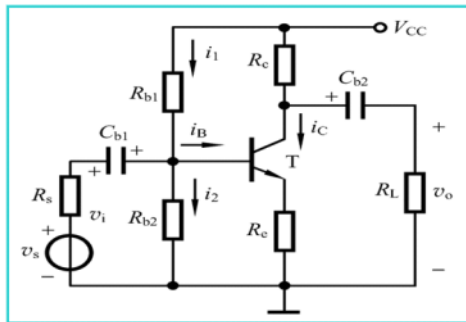

Q point:


$$V_{BQ} \approx \frac{R_{b2}}{R_{b1} + R_{b2}} \cdot V_{CC}$$

$$I_{CQ} \approx I_{EQ} = \frac{V_B - V_{BEQ}}{R_e}$$



$$I_{BQ} = \frac{I_{CQ}}{\beta}$$

$$V_{CEQ} \approx V_{CC} - I_{CQ}(R_c + R_e)$$

DC circuit

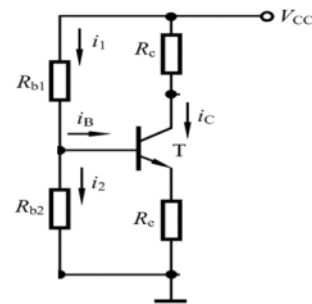

For a more complicated BJT circuit:

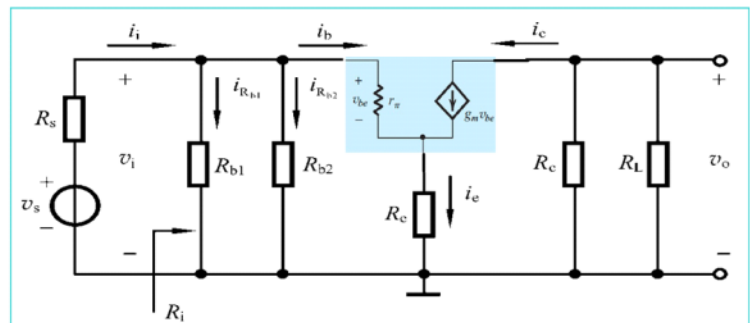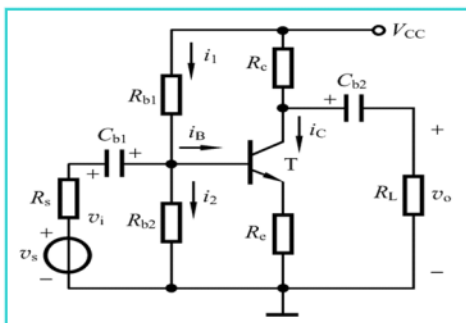

AC circuit

$$v_i = v_{be} + i_e R_e = i_b r_\pi + i_e R_e = i_b r_\pi + (1 + \beta) i_b R_e$$

$$i_c = g_m v_{be} = g_m i_b r_\pi = g_m i_b \beta / g_m = \beta i_b$$

$$v_o = -i_c \cdot \left(\frac{R_c R_L}{R_c + R_L} \right)$$

$$A_v = \frac{v_o}{v_i} = \frac{-i_c \cdot \left(\frac{R_c R_L}{R_c + R_L} \right)}{i_b r_\pi + (1 + \beta) i_b R_e} = - \frac{\beta \cdot R_c R_L}{(r_\pi + (1 + \beta) R_e)(R_c + R_L)}$$

Blackboard Notes for lecture 4

slide 4:

the slope of the straight line will contribute to different Q point.

slide 7:

the Q point should be properly selected, otherwise, it will result in waveform distortion.

slide 8:

$$A_v = - \frac{\beta \cdot R_c \cdot R_L}{h_{\pi}(R_c + R_L)}, \text{ be aware of the minus sign here,}$$

it means the ~~phase~~ output signal and input signal are out of phase (180° phase difference).

the amplification coefficient can be tuned by adjusting the values of R_c and R_L .

slide 9:

please be aware of i_b which is generally not equal to i_B . calculate input impedance and output impedance according to definitions.

slide 17:

for any complicated BJT circuit:

you need to formulate v_i and v_o , then


$$\text{calculate } A_v = \frac{v_o}{v_i}$$

Also, DC circuit should be first drawn to determine Q point.

then AC circuit should be built to formulate v_i and v_o .


Practice Exercise _Lecture 4

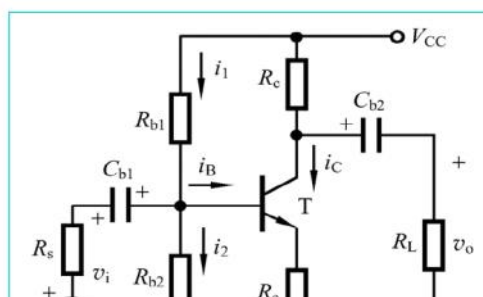1. For the following circuit, $V_{CC} = 16 \text{ V}$, $R_{b1} = 56 \text{ k}\Omega$, $R_{b2} = 20 \text{ k}\Omega$, $R_c = 2 \text{ k}\Omega$, $R_e = 3.3 \text{ k}\Omega$, $R_L = 6.2 \text{ k}\Omega$, $R_s = 500 \Omega$, $\beta = 80$, $V_{BEQ} = 0.7 \text{ V}$.



Practice Exercise _Lecture 4

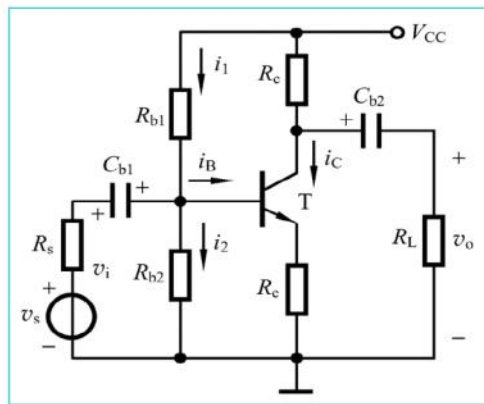1. For the following circuit, $V_{CC} = 16\text{ V}$, $R_{b1} = 56\text{ k}\Omega$, $R_{b2} = 20\text{ k}\Omega$, $R_c = 2\text{ k}\Omega$, $R_e = 3.3\text{ k}\Omega$, $R_L = 6.2\text{ k}\Omega$, $R_s = 500\text{ }\Omega$, $\beta = 80$, $V_{BEQ} = 0.7\text{ V}$.




- Draw its corresponding DC circuit, and calculate the Q operating point.
- Draw its corresponding small-signal model, and calculate R_i , R_o , and A_v .
- If a capacitor with a value of $50\mu\text{F}$ is parallel with R_e , please calculate (a) and (b) again.

Answers to practice exercise of lecture 4

a. DC circuit:

C becomes open!

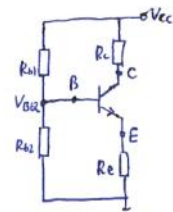

$$V_{BQ} \approx \frac{R_{b2}}{R_{b1} + R_{b2}} \cdot V_{CC} = 4.21\text{ V}$$

$$I_{CQ} \approx I_{EQ} = \frac{V_{BQ} - V_{BEQ}}{R_e} = 1.755\text{ mA}$$


$$V_{CEQ} = V_{CC} - I_{CQ}R_c - I_{EQ}R_e \approx V_{CC} - I_{CQ}(R_c + R_e) = 6.69\text{ V}$$

$$I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{1.755\text{ mA}}{80} = 21.9\text{ }\mu\text{A}$$

$$Q (21.9\text{ }\mu\text{A}, 1.755\text{ mA}, 6.69\text{ V})$$

b. C becomes short's here!

fi

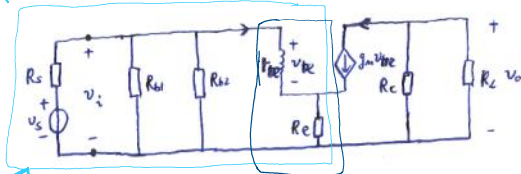

$$R_i = R_{b1} \parallel R_{b2} \parallel [r_{be} + (1 + \beta)R_e] \approx 13.5\text{ k}\Omega$$

$$r_{be} = \frac{\beta}{g_m}, \quad g_m = \frac{I_{CQ}}{V_T} = \frac{1.755\text{ mA}}{26\text{ mV}} = 0.0675\text{ S}$$

$$r_{be} = \frac{80}{0.0675} \approx 1185\text{ }\Omega = 1.185\text{ k}\Omega$$

$$R_o \approx R_c = 3.3\text{ k}\Omega$$

$$A_v = \frac{v_o}{v_i} = - \frac{\beta \cdot (R_c \parallel R_L)}{r_{be} + (1 + \beta)R_e} \approx -1.05$$

Remember this!

$$R_o = \frac{V_a}{I_c}$$


V_a = early voltage effect

$$15 < V_a < 200$$

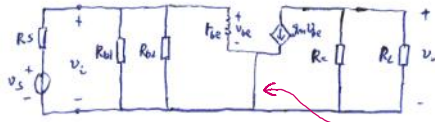c. if a capacitor is parallel with R_e , ~~the circuit is~~

the Q point is the same as the capacitor is regarded as open in DC circuit. AKA R_e disappears

recalculate i_{BQ} , since capacitor is regarded as short for AC circuit.



$$R_i = R_{b1} \parallel R_{b2} \parallel r_{be} \approx 1.1 \text{ k}\Omega$$

$$R_o = R_c = 3.3 \text{ k}\Omega$$

$$A_v = \frac{v_o}{v_i} = - \frac{\beta \cdot (R_c \parallel R_L)}{r_{be}} \approx -995$$

$R_c \parallel C = 0$
as C are short for this model


This is a mistake!
should be $R_c \parallel R_L$

check this again, yes


... Calculations done by us ...

Practice Exercise _Lecture 4

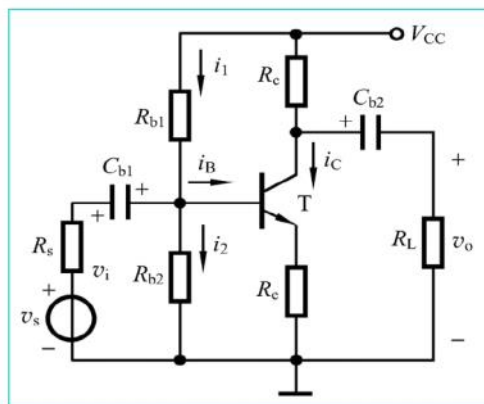- For the following circuit, $V_{CC} = 16 \text{ V}$, $R_{b1} = 56 \text{ k}\Omega$, $R_{b2} = 20 \text{ k}\Omega$, $R_e = 2 \text{ k}\Omega$, $R_c = 3.3 \text{ k}\Omega$, $R_L = 6.2 \text{ k}\Omega$, $R_s = 500 \Omega$, $\beta = 80$, $V_{BEQ} = 0.7 \text{ V}$.



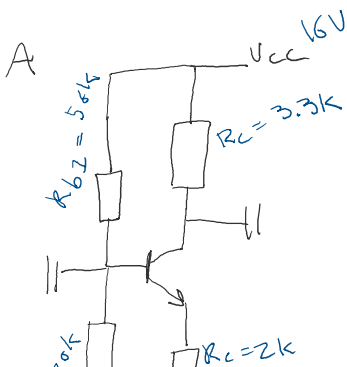
- Draw its corresponding DC circuit, and calculate the Q operating point.
- Draw its corresponding small-signal model, and calculate R_i , R_o , and A_v .
- If a capacitor with a value of $50 \mu\text{F}$ is parallel with R_e , please calculate (a) and (b) again.



Q point (I_{BQ} , I_{CQ} , V_{CEQ})

$$I_{BQ} = \frac{V_{BQ} - V_{BEQ}}{R_B}$$
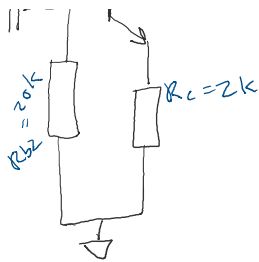
$$V_{BQ} = \frac{R_{b2}}{R_{b2} + R_{b1}} \cdot V_{CC} = 4.2$$



$$V_{BQ} = \frac{R_{b2}}{R_{b1} + R_{b2}} \cdot V_{CC} = 4.2$$



$$R_B = R_{b1} \parallel R_{b2} \parallel \beta \cdot R_E \quad \text{so we can't!}$$

$$I_{EQ} \approx I_{CQ} = \frac{V_{BQ} - V_{BEQ}}{R_E} = \frac{4.2 - 0.6}{2k} = 1.8 \text{ mA}$$

$$I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{1.8 \text{ mA}}{80} = 22.5 \mu\text{A}$$

$$V_{CEQ} = V_{CC} - I_{CQ} \cdot R_C - I_{EQ} \cdot R_E = 16 - 1.8 \text{ mA} \cdot (3.3k + 2k) = 6.46 \text{ V}$$

Q (22.5 μA , 1.8 mA, 6.46 V)

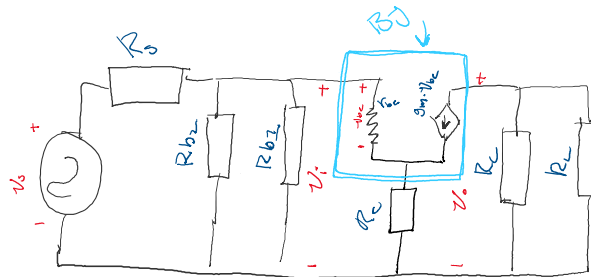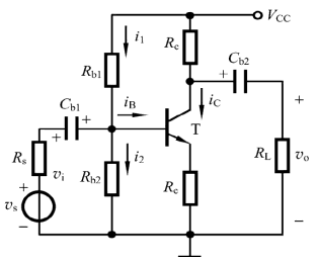

SÅ SKAL VI LIGE HAVE FUNDET NOGEN VARIABLER

$$g_m := \frac{I_{CQ}}{V_T} = 67.51 \times 10^{-3}$$

$$r_{be} := \frac{\beta}{g_m} = 1.19 \times 10^3 \xrightarrow{\text{affix unit ohm}} 1.19 \times 10^3 \Omega$$

Vi bruger faktisk ikke lige R_i , men nu udregner vi den så sku alligevel.

$$R_i := \frac{1}{\frac{1}{R_{b1}} + \frac{1}{R_{b2}} + \frac{1}{(r_{be} + (1 + \beta) \cdot R_E)}} = 13516.22465 \xrightarrow{\text{affix unit ohm}} 13.52 \times 10^3 \Omega$$

Det vigtigste er faktisk hvor sidste "resistor led" da vi genbruger den igen, sener til vores A_V

R_o , skal vi dog bruge og derfor regner vi den nu her.



$$R_o := \frac{1}{\frac{1}{R_C} + \frac{1}{R_E}} = 2153.684211 \xrightarrow{\text{affix unit ohm}} 2.15 \times 10^3 \Omega$$



$$A_V := - \frac{\beta \cdot R_o}{r_{be} + (1 + \beta) \cdot R_E}$$

$$A_V := -1.055824549$$

(1.2.1)

3. a C || R_E

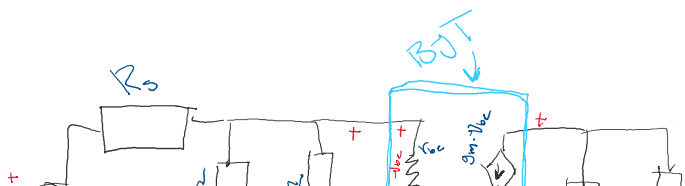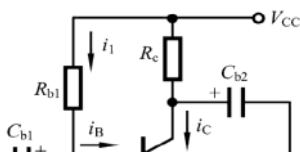

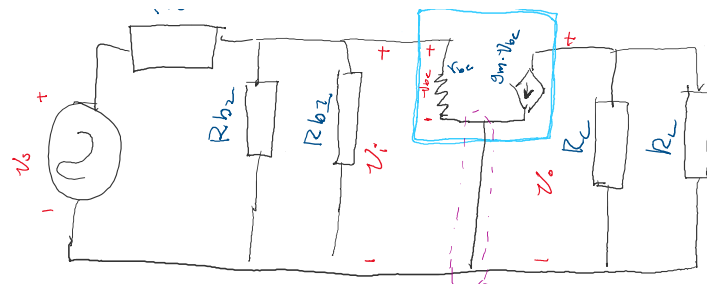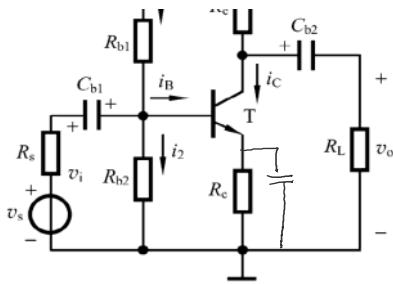

Notice how this has changed

FIND THE Q-POINT

Q (I_{CQ} , I_{EQ} , V_{CEQ})

$$V_{BQ} := \frac{R_{b2}}{R_{b1} + R_{b2}} \cdot V_{CC} = 4.21 \xrightarrow{\text{affix unit volt}} 4.21 \text{ V}$$

$$I_{EQ} := \frac{V_{BQ} - V_{BEQ}}{R_E} = 1.76 \times 10^{-3}$$

Og så siger vi at der roughly er det samme:

$$I_{CQ} := I_{EQ}$$

$$1.76 \times 10^{-3}$$

(1.3.1.1)

$$I_{BQ} := \frac{I_{CQ}}{\beta}$$

$$21.94 \times 10^{-6}$$

(1.3.1.2)

$$V_{CEQ} := V_{CC} - I_{CQ} \cdot R_C - I_{EQ} \cdot R_E$$

$$6.70$$

(1.3.1.3)

$\xrightarrow{\text{affix unit volt}}$

$$6.697105259 \text{ V}$$

(1.3.1.4)

Så er dit Q point altså:

$$I_{BQ}$$

$$21.94 \times 10^{-6}$$

(1.3.1.5)

HVIS DU NU LIGE IKKE HAVDE REGNET DET (DUCKING) UD, SÅ ER DET OVENOVER I AMPERE

$$I_{CQ}$$

$$1.76 \times 10^{-3}$$

(1.3.1.6)

HVIS DU NU LIGE IKKE HAVDE REGNET DET (DUCKING) UD, SÅ ER DET OVENOVER I AMPERE

$$V_{CEQ}$$

$$6.697105259$$

(1.3.1.7)

$$Q(I_{BQ}, I_{CQ}, V_{CEQ})$$

$$Q(21.94 \times 10^{-6}, 1.76 \times 10^{-3}, 6.70)$$

(1.3.1.8)

A new A_V is found

$$g_m := \frac{I_{CQ}}{V_T} = 67.51 \times 10^{-3}$$

Yo, pssst, makker. Husk at $r_{be} = r_\pi$

$$r_{be} := \frac{\beta}{g_m} = 1.19 \times 10^3 \xrightarrow{\text{affix unit ohm}} 1.19 \times 10^3 \Omega$$

$$R_{in} := \frac{1}{\frac{1}{R_{b1}} + \frac{1}{R_{b2}} + \frac{1}{r_{be}}} = 1096.811539$$

$$R_{out} := \frac{1}{\frac{1}{R_C} + \frac{1}{R_L}} = 2153.684211$$

$$A_V := -\frac{\beta \cdot R_{out}}{r_{be}}$$

$$A_V := -145.3954827$$

(1.3.2.1)

Fortegnet er negativt da den er inverterende, husk nu lige det.