

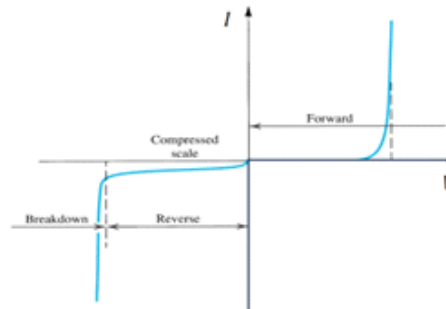


PN junction- forward bias

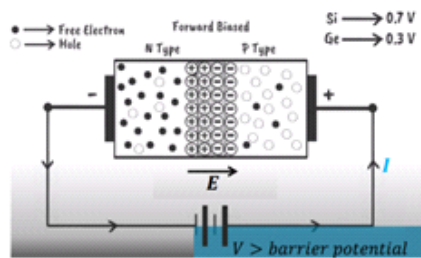

- Battery V pushes the free electrons (majority charge carrier) from N to P.
- As long as the battery can provide current, the current can flow from P to N.
- The current increases dramatically as V increases.
- A 'fully conducting' diode \rightarrow voltage drop is 0.6 V \sim 0.8 V

PN junction- Shockley's equation

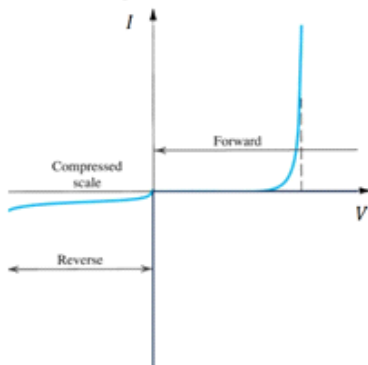

$$I = I_s \left(e^{\frac{V}{nV_T}} - 1 \right) \quad \text{For anything with PN junctions}$$

I_s : reverse saturation current, given in datasheet

V : voltage across the junction

n : ideal factor, depending on the construction of the PN junction, $1 < n < 2$, $n = 1$ for ideal PN junction

V_T : thermal voltage

$$V_T = \frac{KT_K}{q}$$

K : Boltzmann's constant = 1.38×10^{-23} J/K


T_K : the absolute temperature in kelvins = $273 + x^\circ\text{C}$

q : the magnitude of electronic charge = 1.6×10^{-19} C

I_s and V_T are temperature dependent.

I_s doubles for every 5°C rise in temperature. $V_T \approx 26 \text{ mV @ } 27^\circ\text{C}$

PN diode

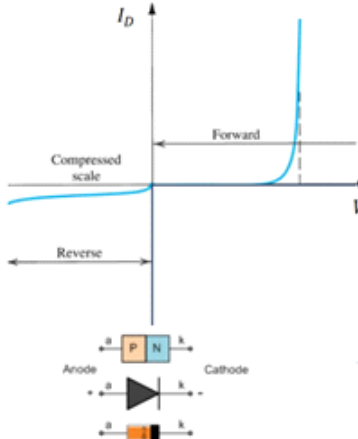

$$I_D = I_s \left(e^{\frac{V_D}{nV_T}} - 1 \right)$$

- I_s : reverse saturation current, given in datasheet
- V_D : voltage across the diode
- n : ideal factor, depending on the diode's construction, $1 < n < 2$, $n = 1$ for ideal diode
- V_T : thermal voltage, $V_T \approx 26 \text{ mV @ } 27^\circ\text{C}$

When a diode is forward-biased:

$$I_D \approx I_s e^{\frac{V_D}{V_T}}$$

- For $V_D \gg V_T$ ($V_D > 4V_T$ in practice), $e^4 \approx 54.5$
- $n = 1$

Lec. 1: assignment 1.1

In the laboratory, 2 sets of related values of current and voltage at two temperatures have been measured for the diode 1N4001:

- At 25°C : $(V_{D1}, I_{D1}) = (540 \text{ mV}, 1 \text{ mA})$, and $(V_{D2}, I_{D2}) = (450 \text{ mV}, 0.1 \text{ mA})$
 - At 75°C : $(V_{D1}, I_{D1}) = (420 \text{ mV}, 1 \text{ mA})$, and $(V_{D2}, I_{D2}) = (315 \text{ mV}, 0.1 \text{ mA})$
- Calculate the constants of the diode equation: n and I_s for each temperature.
 - Calculate the temperature coefficient [mV/K] of the diode at current = 1 mA.

$$I_D \approx I_s e^{\frac{V_D}{nV_T}}$$

$$V_D = nV_T \ln \frac{I_D}{I_s}$$


$$V_{D2} = nV_T \ln \frac{I_{D2}}{I_s} \text{ \& } V_{D1} = nV_T \ln \frac{I_{D1}}{I_s} \Rightarrow n = \frac{V_{D2} - V_{D1}}{V_T \ln \frac{I_{D2}}{I_{D1}}} \text{ \& } I_s = I_{D1} e^{-\frac{V_{D1}}{nV_T}}$$

$$V_T = \frac{kT_K}{q} \rightarrow V_T(25^\circ\text{C}) = 25.7 \text{ mV} \text{ \& } V_T(75^\circ\text{C}) = 30 \text{ mV}$$

$$\text{At } 25^\circ\text{C}: n = \frac{450 \text{ mV} - 540 \text{ mV}}{25.7 \text{ mV} \ln \frac{0.1 \text{ mA}}{1 \text{ mA}}} = 1.52 \text{ \& } I_s = 1 \text{ mA} e^{-\frac{540 \text{ mV}}{1.52 \cdot 25.7 \text{ mV}}} = 1 \text{ nA}$$

$$\text{At } 75^\circ\text{C}: n = \frac{315 \text{ mV} - 420 \text{ mV}}{30.0 \text{ mV} \ln \frac{0.1 \text{ mA}}{1 \text{ mA}}} = 1.52 \text{ \& } I_s = 1 \text{ mA} e^{-\frac{420 \text{ mV}}{1.52 \cdot 30.0 \text{ mV}}} = 100 \text{ nA}$$
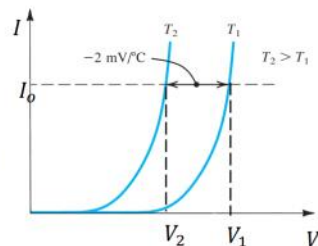
$$\frac{\Delta V_D}{\Delta T} = \frac{420 \text{ mV} - 540 \text{ mV}}{75^\circ\text{C} - 25^\circ\text{C}} = -2.4 \text{ mV/}^\circ\text{C}$$




Kursusl ninger

Lec. 1: assignment 1.2 –ideal model

No/Neg voltage


Voltage is on

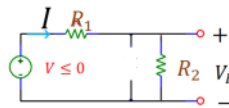

$$I = I_{R2} = V / (R_1 + R_2)$$

$$V_{R1} = V R_1 / (R_1 + R_2)$$

$$V_D = V_{R2} = V R_2 / (R_1 + R_2)$$


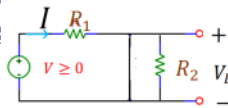


$$I = V / R_1$$


$$I_{R2} = 0$$

$$V_{R1} = I R_1 = V$$

$$V_D = V_{R2} = 0$$

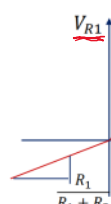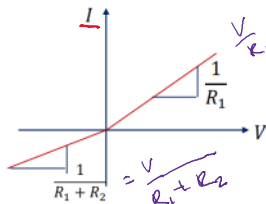


Lec. 1: assignment 1.2 –ideal model

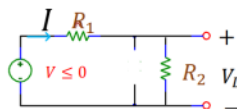

$$I = I_{R2} = V / (R_1 + R_2)$$

$$V_{R1} = V R_1 / (R_1 + R_2)$$

$$V_D = V_{R2} = V R_2 / (R_1 + R_2)$$


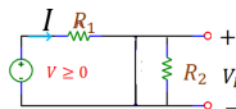


$$I = V / R_1$$


$$I_{R2} = 0$$

$$V_{R1} = I R_1 = V$$

$$V_D = V_{R2} = 0$$

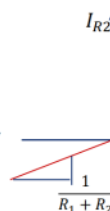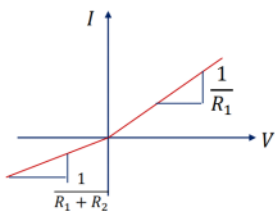

Lec. 1: assignment 1.2

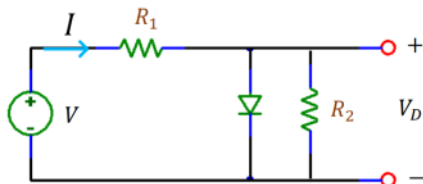


2. Constant voltage drop model

Draw the equivalent circuit and calculate I , I_{R2} , V_{R1} , V_D and V_{R2}

- When $V < V_{D,on}$
 - When $V = V_{D,on}$
 - When $V = \frac{R_1 + R_2}{R_2} V_{D,on}$
 - When $V > \frac{R_1 + R_2}{R_2} V_{D,on}$
- The I - V curve.
 - The I_{R2} - V curve.
 - The I_D - V curve.
 - The V_{R1} - V curve, with V_{R1} denoting the voltage across $R1$.
 - The V_D - V curve, with V_D denoting the voltage across diode.

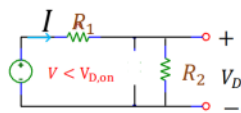Lec. 1: assignment 1.2 –constant voltage drop




$$V < V_{D,on}$$

$$I = I_{R2} = V / (R_1 + R_2)$$

$$V_{R1} = V R_1 / (R_1 + R_2)$$

$$V_D = V_{R2} = V R_2 / (R_1 + R_2)$$

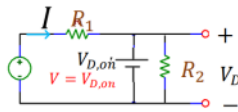

If we assume $V = V_{D,on}$, the diode is on \rightarrow the voltage drop

across R_1 will be 0 $\rightarrow I = 0$ (1)

The diode is about to turn on $\rightarrow I_D = 0$

$$\text{However, } I_{R2} = \frac{V_{D,on}}{R_2} \neq 0$$

$$\text{And } I = I_D + I_{R2} \neq 0 \text{ (2)}$$


(1) And (2) conflicts \rightarrow the diode should be off \rightarrow same results as for $V < V_{D,on}$

$$I = I_{R2} = V / (R_1 + R_2)$$

$$V_{R1} = V R_1 / (R_1 + R_2)$$

$$V_D = V_{R2} = V R_2 / (R_1 + R_2)$$

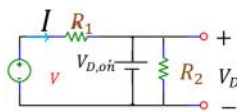Lec. 1: assignment 1.2 –constant voltage drop



$$V = \frac{R_1 + R_2}{R_2} V_{D,on}$$

$$\text{If we assume } V = V_{D,on}, \text{ the diode is on } \rightarrow I = \frac{V - V_{D,on}}{R_1} = \frac{V_{D,on}}{R_2}$$

(1)

The diode is about to turn on $\rightarrow I_D = 0$

$$\text{And, } I_{R2} = \frac{V_{D,on}}{R_2}$$

$$\text{And } I = I_D + I_{R2} = \frac{V_{D,on}}{R_2} \text{ (2)}$$


(1) And (2) true \rightarrow the diode should be on

$$I = I_{R2} = \frac{V_{D,on}}{R_2}$$

$$V_{R1} = I R_1 = \frac{R_1 V_{D,on}}{R_2}$$

$$V_D = V_{R2} = V_{D,on}$$

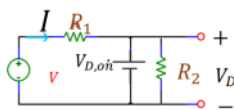Lec. 1: assignment 1.2 –constant voltage drop



$$V > \frac{R_1 + R_2}{R_2} V_{D,on}$$

$$\text{the diode is on } \rightarrow I = \frac{V - V_{D,on}}{R_1}$$


$$I_{R2} = \frac{V_{D,on}}{R_2}$$

$$I_D = I - I_{R2} = \frac{V - V_{D,on}}{R_1} - \frac{V_{D,on}}{R_2}$$


$$V_{R1} = I R_1 = V - V_{D,on}$$

$$V_D = V_{R2} = V_{D,on}$$

Lec. 1: assignment 1.2 –constant voltage drop

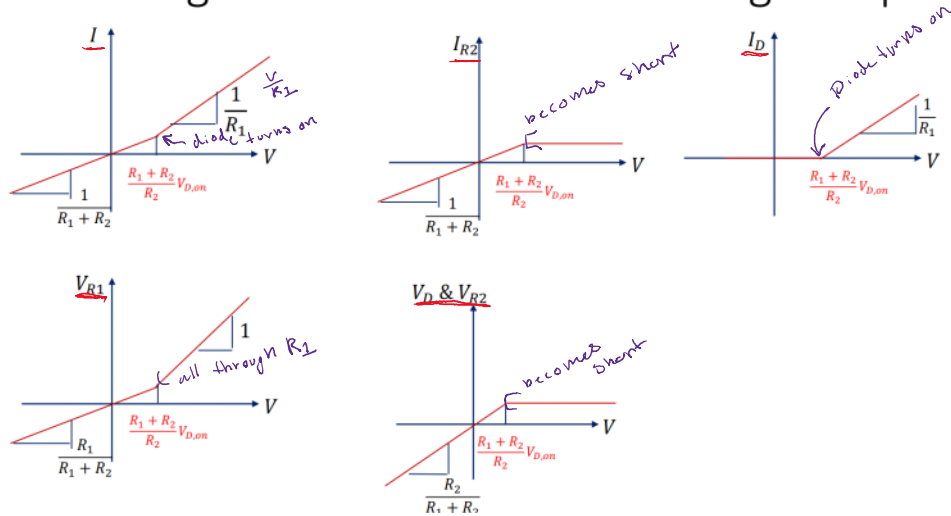

Lec. 1: assignment 1.3

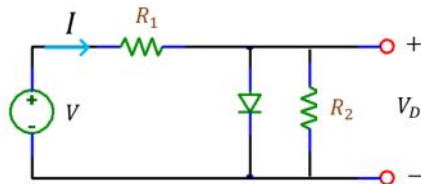

Assuming the constant voltage drop model and the diode in reverse and forward bias regions,

- The I - V curve.
- The I_{R2} - V curve.
- The I_D - V curve.
- The V_{R1} - V curve, with V_{R1} denoting the voltage across R_1 .
- The V_D - V curve, with V_D denoting the voltage across diode.
- The V_{R2} - V curve, with V_{R2} denoting the voltage across R_2 .

